

BANGLADESH SCHOOL & COLLEGE

Sultanate of Oman

Physics 2nd Paper

Practical Notebook




Sultanate of Oman

Physics 2nd Paper


Designed by
W4H1D

Class: Eleven - Twelve

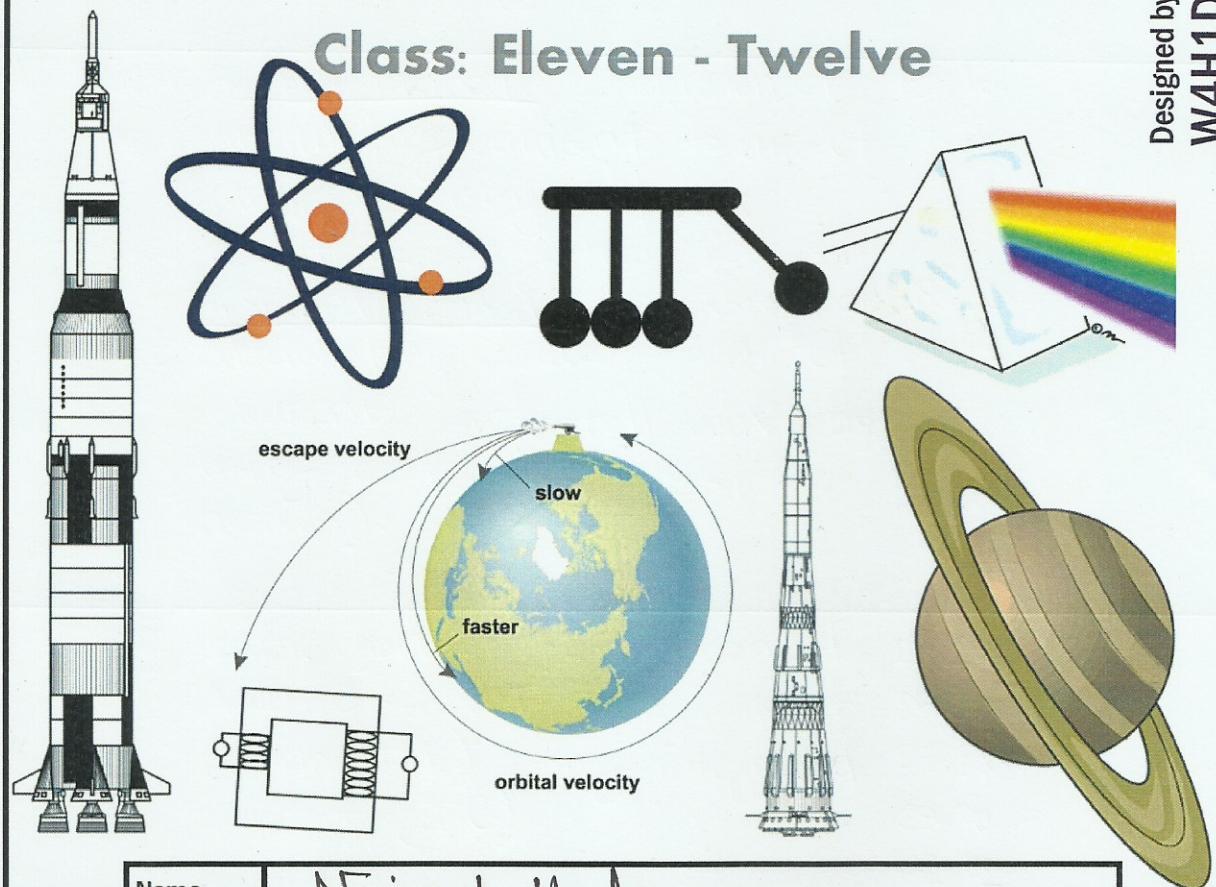

Name	Najmul Huda	
Roll no.		Reg. no.
Session	2020 - 2021	
Board	Dhaka	

BALANCE

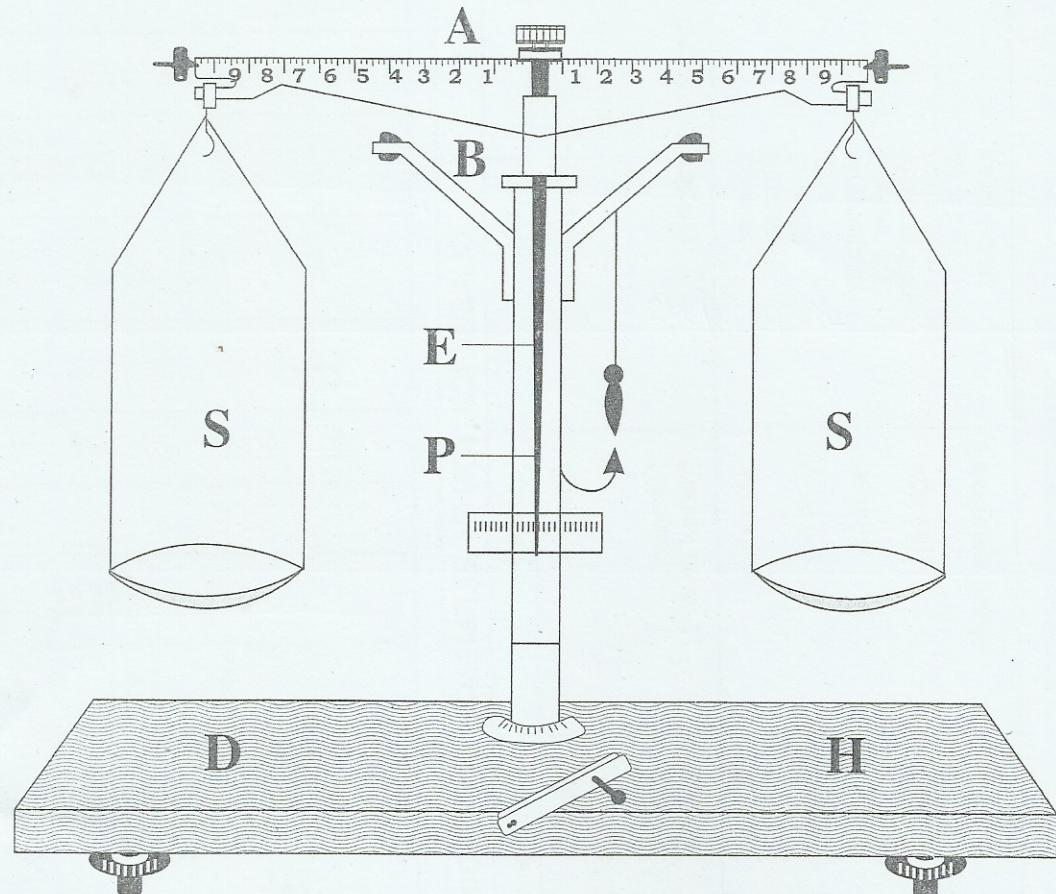

A= METALLING BEAM

D= WOODEN FRAME

H= HANDLE

B= MOVABLE ROD

E= POINTER

P= PILLER, S= BALANCE PANS

NAME : Najmul Huda

SCHOOL/ COLLEGE : Bangladesh School & College, Saham

SUBJECT : Physics 2nd paper

ROLL NO. :

SESSION : 2020 - 2021

REGISTRATION NO. :

USEFUL DATA FOR PHYSICS

SI NO	NAME OF ELEMENTS	SPECIFIC			LATENT HEAT	THERMAL CONDUCTIVITY	VELOCITY OF SOUND	REFRACTIVE INDEX	CRITICAL ANGLE	BREAKING STRESS	MODULUS OF RIGIDITY	YOUNGS MODULIUS	CO-EFFICIENT EXPANSION		
		GRAVITY	RESISTANCE	HEAT											
1	COPPER	8.93	1.78	0.091-0.094	-	50.6	-	-	-	-	30,000	3.9-40X10 ¹¹	12.4-12.8X10 ¹¹	0.000167	-
2	BRASS	8.6	4.156	0.088-0.092	-	65.0	-	-	-	-	36,000	3.5X10 ¹¹	9.9-10.2X10 ¹¹	0.000189	-
3	IRON (-OUS)	7.2	13.19-18.80	0.119	-	-	-	-	-	-	34,000	7.7-8.3X10 ¹¹	0.000102	-	
4	IRON (IC)	7.86	12.0-16.80	-	-	-	-	-	-	-	8,000	7.9-8.9X10 ¹¹	19.9-20X10 ¹¹	0.00023	-
5	STEEL	26.27	3.21	0.21	-	-	-	-	-	-	5200	-	10-13X10 ¹¹	0.0000258	-
6	ALUMINUM	7.1	6.10	0.033	-	93.0	-	-	-	-	-	-	-	0.0000291	-
7	ZINC	11.4	20.80	0.109	-	24.1	-	-	-	-	-	-	-	0.000128	-
8	LEAD	-	-	-	-	5.4	-	-	-	-	-	-	-	-	-
9	NICKEL	8.9	-	-	-	0.056	-	-	-	-	-	-	-	-	-
10	SILVER	-	-	-	-	0.14200	-	-	-	-	-	-	-	-	-
11	GOLD	19.3	-	0.033	-	21.0	-	-	-	-	-	-	-	-	-
12	PLATINUM	21.5	1.63	0.055	-	0.16	-	-	-	-	-	-	-	-	-
13	MERCURY	-	-	-	-	1.12	-	-	-	-	-	-	-	-	-
14	TIN	2.29	11.00	0.16	-	14.0	-	-	-	-	0.02000	-	-	0.000089	-
15	GLASS (FUNT)	2.9-5.9	-	-	-	0.42	-	-	-	-	5000-5300	-	-	0.000214	-
16	GLASS (CROWN)	2.4-2.8	11.30	-	-	1.51	-	-	-	-	153-180	41.25	-	-	-
17	TARANTINE OIL	0.87	-	-	-	1.00	-	-	-	-	137.0	41.45	-	-	-
18	ALCOHOL (ETHYL)	0.79	-	-	-	5.37	-	-	-	-	1260.0	43.15	-	-	-
19	WATER	-	-	0.502	-	0.58	-	-	-	-	14.10	43.15	-	-	-
20	ICE	0.92	-	-	-	80.0	-	-	-	-	-	-	-	-	-
21	GLYCERINE	1.28	-	-	-	-	-	-	-	-	-	-	-	-	-
22	KEROSENE	0.98	-	-	-	-	-	-	-	-	-	-	-	-	-
23	RUBBER	0.9-13	-	-	-	-	-	-	-	-	0.0045	30-40	-	-	-

CLASSIFICATION OF ELEMENTS ACCORDING TO THEIR VALENCY

Mono valent	Divalent	Trivalent	Tetravalent	Panta Valent	Hexavalent
Hydrogen	Oxygen	Boron	Carbon	Nitrogen	Sulphur
Fluorine					
Chlorine					
Bromine					
Iodine					
Potassium	Calcium	Nitrogen	Silicon		
Sodium	Strontium	Phosphorus	Supphur		
	Barium				
Zinc	Gold (ic)				
Mercury (ous)	Magnesium				
Copper (-ous)	Copper (ic)				
Iron (-ous)	Iron (-ic)				
tin (-ous)	Tin (-ic)				
Lead (-ous)	Lead				
Silver		Antimony (-ous)			

PRACTICAL


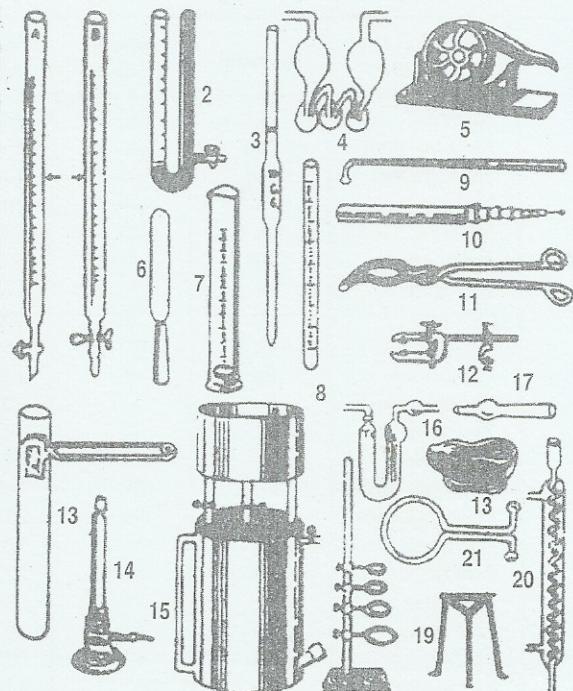


PLATE NO.1

- | | |
|-----------------------|-----------------------------------|
| 1. BURETTE | 12. CLAMP |
| 2. EUDIOMETER | 13. TEST TUBE WITH HOLDER |
| 3. PIPETTE | 14. BUNSEN BUENER |
| 4. POTASH BULES | 15. GAS HOLDER |
| 5. CORK SQUEEZER | 16 & 17. Ca Cl ₂ -TUBE |
| 6. SPATULA | 18. MERCURY TROUGH |
| 7. MEASURING CYLINDER | 19. TRIPOD STAND |
| 8. MEASURING TUBE | 20. CONDENSER |
| 9. BLW PIPE | 21. CLIP |
| 10. CORK BORER | 22. RETORT STAND |
| 11. TONGS | |

PLATE NO. 2

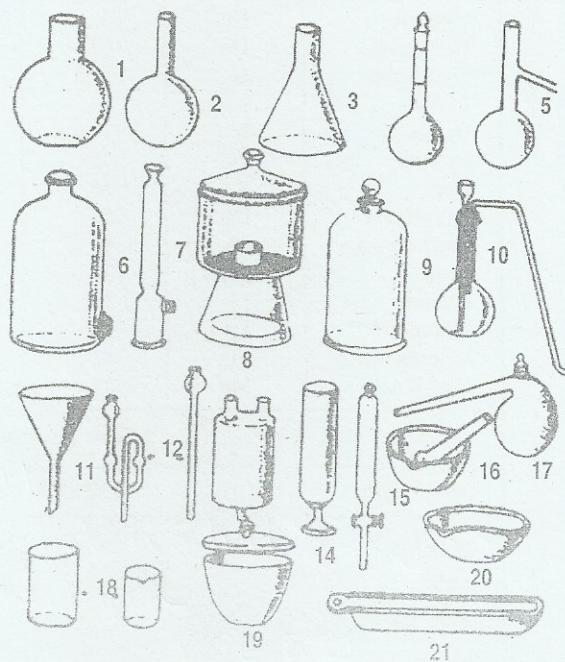1. FLAT BOTTOM FLASK
2. ROUND BOTTOM FLASK
3. CONICAL FLASK
4. MEASURING FLASK
5. DISTILLING FLASK
6. ASPIRATOR
7. TOWER
8. DESICCATOR
9. BELL JAR
10. FLASK WITH THISTLE FUNNEL & DELIVERY TUBE
11. FUNNEL
12. THISTLE FUNNELS
13. WOULFEE'S BOTTLE
14. TEST GLASS
15. SEPARATING FUNNEL
16. MORTAR & PESTLE
17. BETORT
18. BEAKERS
19. CRUCIBLE
20. BASIN
21. BOAT





ATOMIC NUMBERS AND ATOMIC WEIGHTS WITH THEIR SYMBOLS

Name of the Element	Symbol	Atomic Number	Atomic Weight	Name of the Element	Symbol	Atomic Number	Atomic Weight
Actinium	Ac	89	227	Mercury	Hg	80	200.5
Aluminium	Al	13	6.97	Molybdenum	Mo	42	95.9
Amercium	Am	95	243	Neodymium	Nd	60	144.2
Antimony	Sb	51	121.7	Neon	Ne	10	20.17
Aragon	Ar	18	39.94	Nickel	Ni	28	58.7
Arsenic	As	33	74.9216	Niobium	Nb	41	92.9064
Astatine	At	85	210	Nitrogen	N	7	14.0067
Barium	Ba	56	137.3	Osmium	Os	76	190.2
Berkelium	Bk	97	249	Oxygen	O	8	15.999
Beryllium	Be	56	137.36	Palladium	Pd	46	106.4
Bismuth	Bi	4	9.02	Phosphorus	P	15	30.97376
Boron	B	83	209.00	Platinum	Pt	78	195.0
Bromine	Br	5	10.82	Potassium	K	19	39.09
Cadmium	Cd	35	80	Praseodymium	Pr	59	140.9077
Calcium	Ca	48	11.24	Prtactinium	Pa	91	231.0359
Carbon	C	20	40	Radium	Ra	88	226.0254
Cerium	Ce	6	12	Radom	Rn	86	222
Caesium	Cs	58	140.12	Rhenium	Re	75	186.2
Chlorine	Cl	55	132.91	Rhodium	Rh	45	102.9055
Chromium	Cr	17	35.476	Ruthenium	Ru	44	101.75
Copper	Cu	29	63.5	Rubinium	Rb	37	85.43
Dysprocium	Dy	66	162.46	Samarium	Sun	62	150.4
Erbrium	Er	68	167.67	Seandium	Sc	21	44.9559
Europium	Eu	63	152.0	Selenium	So	34	78.09
Fluorine	F	9	19.00	Sillcon	Si	14	28.08
Franeium	Fr	87	223	Silver	Ag	47	107.868
Gadolinium	Gd	64	156.9	Sodium	Na	11	22.98977
Gaflium	Ga	31	62.72	Stontlum	Sr	38	87.62
Germanium	Ge	32	72.62	Sulphur	S	16	32.06
Gold	Au	79	797.2	Tuntalum	Ta	73	180.947
Hafnium	Hf	72	178.6	Tellurim	Te	52	127.6
Helium	He	2	4.002	Terbium	Th	65	159
Hokmium	Ho	67	163.5	Thallium	Ti	81	20.39
Hydrogen	H	1	1.007	Thorium	Th	90	232.12
Indium	I	53	126.92	Thulium	Tm	69	169.04
Iodine	Ir	77	193.1	Tin	Sm	50	119
Iridium	Fe	26	55.84	Titanium	Ti	22	47.90
Iron	Kr	36	83.7	Tungstem	W	74	184.0
Krypton	La	57	138.9	Uranium	U	92	238.07
Ianthenum	Ph	82	207.22	Vonadium	V	28	50.95
Lead	Lm	3	6.940	Xenon	Xe	54	131.3
Lithium	Li	3	6.94	Ytterubim	Yb	70	178.0
Lutecium	Lu	71	174.97	Yttrium	Y	39	88.9059
Magnecium	Mg	12	24.305	Zunc	Zn	30	65.38
Manganese	Mn	25	54.9380	Zircontum	Zr	40	91.22

তড়িৎ কোষের বৈদ্যুতিক চাপ (E.M.F of Cells)


কোষের নাম	বৈদ্যুতিক চাপ ভোল্ট	কোষের নাম	বৈদ্যুতিক চাপ ভোল্ট
ড্যানিয়েল	1.07-1.08	ড্যানিয়েল	2.0000
বুলসেন	1.08-1.90	বুলসেন	1.8-1.9000
গেকল্যান্স	1.45	গেকল্যান্স	1.433
শুঙ্ক	1.50	শুঙ্ক	1.01830
সেকেভারী		সেকেভারী	
সৌমা এডিস (সঞ্চয়ী)	1.9-2.20	সৌমা এডিস (সঞ্চয়ী)	1.1-1.4000

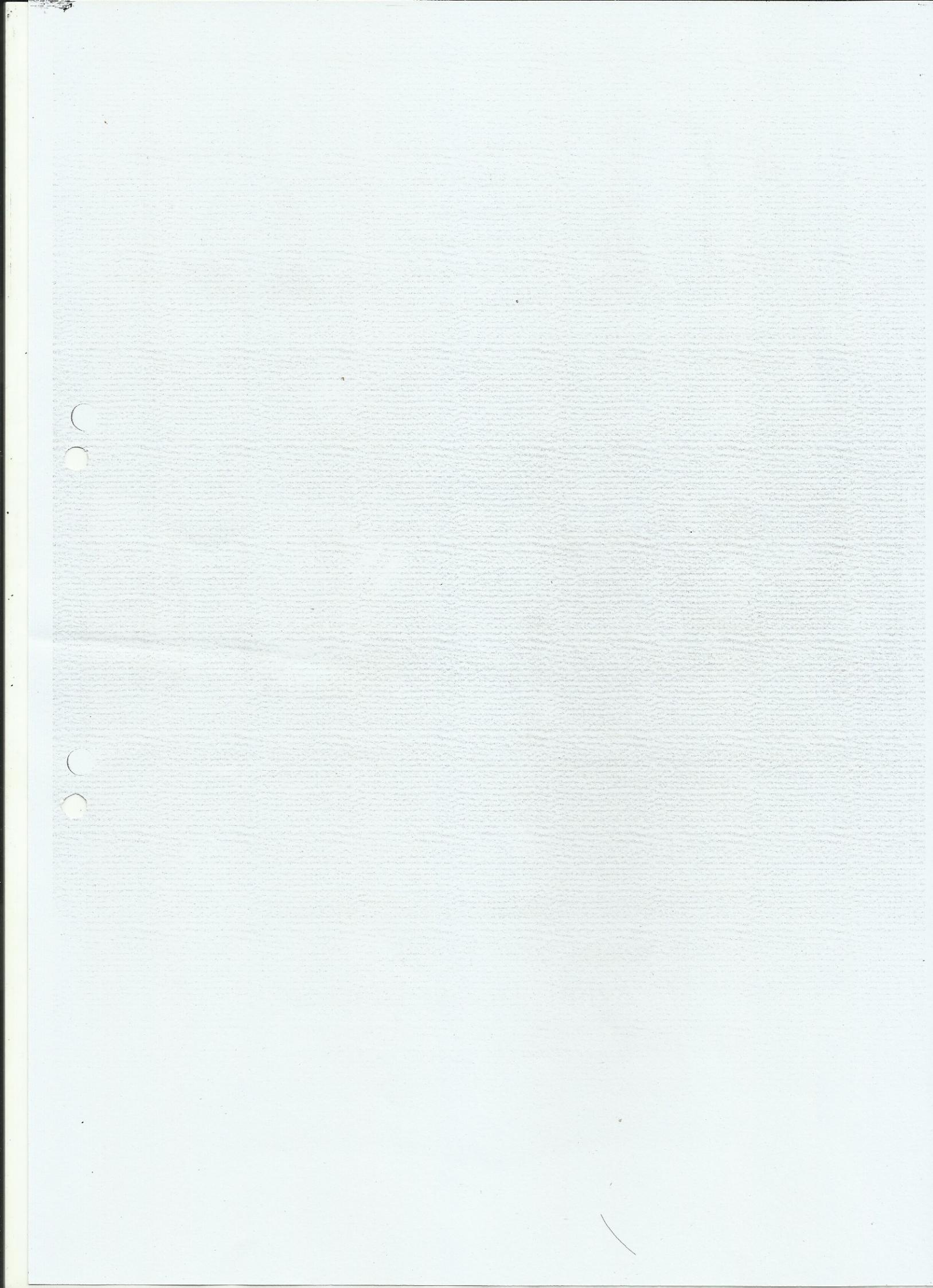

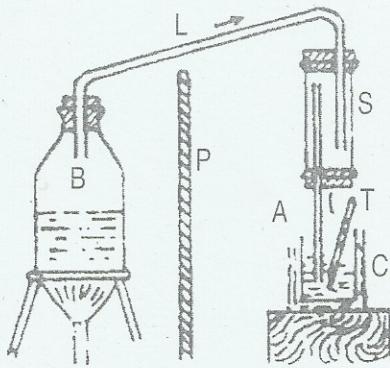


B- Water vessel
 S- Steam trap
 P- A screen
 C- Calorimeter
 T-Thermometer
 A-Exit tube

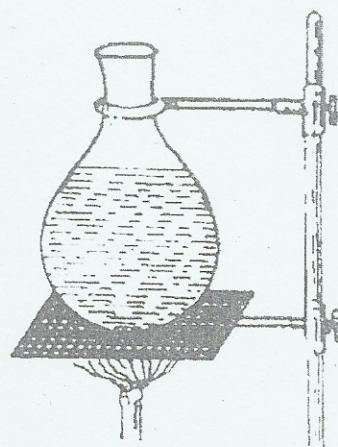
DETERMINATION OF LATENT HEAT
 OF VAPORIZATION OF WATER



TRANSMISSION OF HEAT

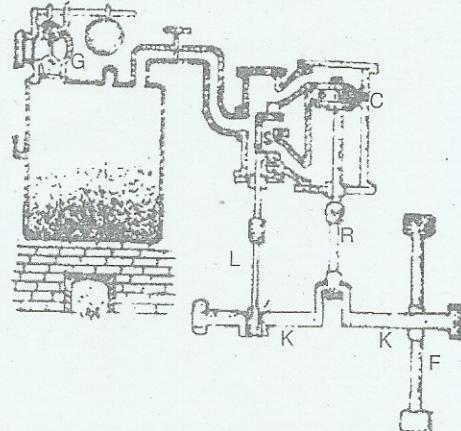

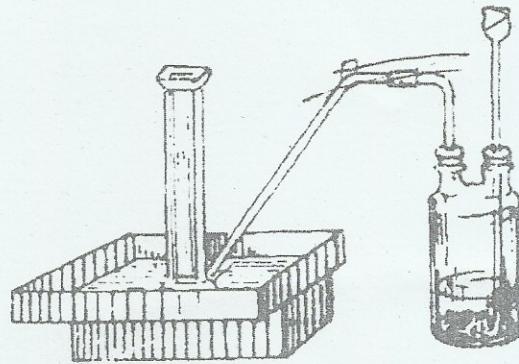SECTIONAL DIAGRAM OF COMPLETE
 STEAM OF ENGINES



LABORATORY METHOD PREP
 OF HYDROGEN

Victoria

Aynal Book Binder

2/3, Jumrail Lane, (Babu Bazar), Dhaka-1100
 Phone : 7395827, 01715787454, 01733160341

Index

Sl. No.	Date	Name of the Experiment	Page No.	Initials	Remarks
01	22/04/2022	Determination of Mechanical equivalent of Heat.	01, 02, 03, 04, 05		
02	24/04/2022	Comparison of E.M.F. of two cells using potentiometer.	06, 07, 08, 09		
03	24/04/2022	Determination of specific resistance of a wire using meter bridge.	10, 11, 12, 13, 14.		
04	25/04/2022	A. First Method: - Conversion of alternating current to direct current using full wave rectifier using two diodes. B. Second method: Conversion of alternating current to direct current using full wave by using bridge rectifier (4 diodes).	15, 16, 17, 18 19, 20, 21, 22		
05	25/04/2022	Verification of the function of AND, OR, NOT gate circuit (Truth table) using integrated circuit (I.C.)	23, 24, 25, 26, 27, 28, 29, 30 31, 32		

Index

This is to Certify that Mr./Miss

A Student of Class Roll No. Has Performed the Required

Number of Experiments in Physics/Chemistry Laboratory of

School/College/University as per Syllabus During the Session

Head of the Department Physics/Chemistry

Determination of Mechanical equivalent of Heat.

PAGE NO. 01

EXPT. NO. 01

Theory:

When a current of strength i flows for t second through a coil of wire of resistance R producing a drop of potential V across it, the work done, $W = Vit = i^2 R t$ Joule.

If all this work is converted into heat, Then from first law of thermodynamics, we know, "Heat and work is proportional to each other". that is $W \propto H$ or $W = JH$; where J = a constant of proportionality.

It is called mechanical equivalent of Heat.

$$\therefore J = \frac{W}{H} = \frac{Vit \text{ (or } i^2 Rt\text{)}}{H} \text{ Joule/cal} \dots\dots (1)$$

Let, the resistance coil be dipped in a liquid of mass m_1 and specific heat s_1 contained in a calorimeter of mass m with stirrer, then

$$H = (ms + m_1 s_1)(\theta_2 - \theta_1) \dots\dots (2)$$

where, s = specific heat of the material of the calorimeter.

$$\therefore \text{From (1) and (2), we get, } J = \frac{Vit \text{ or } i^2 Rt}{(ms + m_1 s_1)(\theta_2 - \theta_1)} \frac{\text{Joule}}{\text{cal}} \dots\dots (3)$$

Apparatus:-

Joule's electrical calorimeter, ammeter, voltmeter, thermometer, battery, key, stop-watch, rheostat, turpentine oil (turpentine), balance, weight box, connecting wire, sand paper etc.

Procedure:

- At first, the calorimeter was dried, cleaned and then was weighed with the stirrer. Let the mass was m .

FIGURE NO. 01

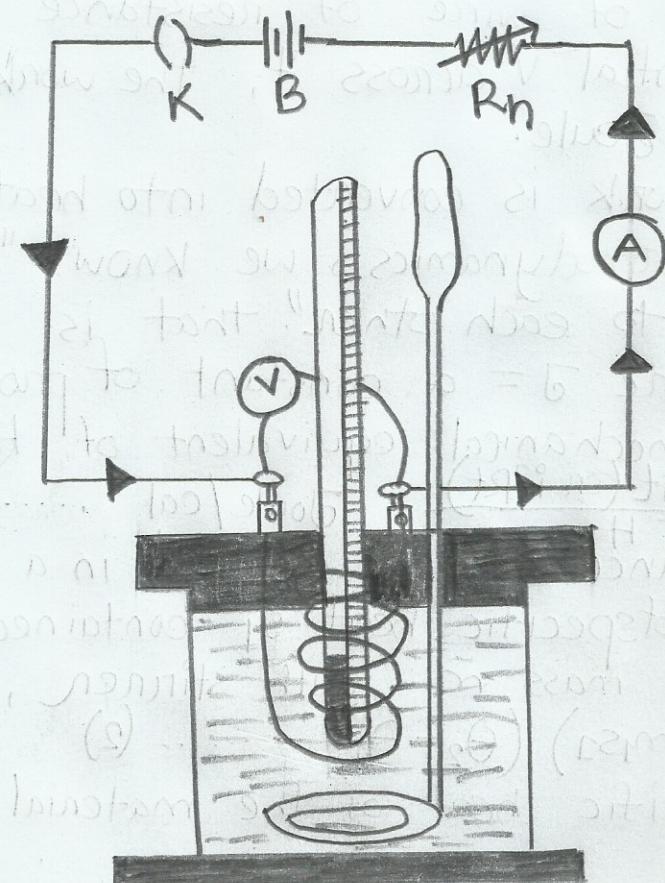


Figure - 01 (Exp - 01): Determination of Mechanical Equivalent of Heat.

Determination of Mechanical equivalent of Heat.

- 2) Now $\frac{2}{3}$ rd of the calorimeter was filled with the liquid and then was weighed. Subtracting the weight m from this weight, the weight (mass) of the liquid (m_1) was obtained.
- 3) The initial temperature (θ_1) of the liquid was determined by a sensitive thermometer.
- 4) Now the calorimeter was included in the circuit and a key (K), a battery (B), a variable resistor (R_h), an ammeter - all were connected in series. Voltmeter (V) was connected in parallel with the coil of the wire.
- 5) Now the circuit was closed (ON) and instantaneously the stop-watch was started. When the temperature of the liquid was raised to about $(5-8)^\circ\text{C}$ [θ_2], then the circuit was opened (OFF). The ammeter and voltmeter readings were taken every minute.
- 6) Then the temperature of the liquid was allowed to come down during the same time and the final temperature (θ_3) was noted. This time always the stirrer was stirred and the temperature was noted every minute also.
- 7) To get the correct rise of temperature of the liquid of the calorimeter, correction of radiation was done. Let the fall of temperature, $n = (\theta_2 - \theta_3)$ $\therefore \frac{1}{2}n = \frac{1}{2}(\theta_2 - \theta_3)$.

\therefore Actual rise of temperature (with radiation correction)

$$\Theta = (\theta_2 - \theta_1) + \frac{1}{2}(\theta_2 - \theta_3)$$

Determination of Mechanical equivalent

of Heat.

Experimental data :-Mass of calorimeter with stirrer, $m = 89.5 \text{ gm}$.Specific heat of the material of the calorimeter, $s = 0.21 \text{ cal gm}^{-1} \text{ }^{\circ}\text{C}^{-1}$ Mass of liquid, $m_1 = 113.3 \text{ gm}$ $\text{cal gm}^{-1} \text{ }^{\circ}\text{C}^{-1}$ Specific heat of liquid, $s_1 = 0.41 \text{ cal gm}^{-1} \text{ }^{\circ}\text{C}^{-1}$ Table (i) : Flow of the current was made ON / closed :-

No. of Observations	Time (min)	Ammeter readings i (Amp)	Voltmeter readings V (Volt)	Temperature ${}^{\circ}\text{C}$
01	0			$29 = \Theta_1$
02	1			29.9
03	2	1.6	3.2	30.8
04	3			31.7
05	4			32.5
06	5			33.3
07	6			$34 = \Theta_2$

Table - (ii) :- Flow of current was made OFF / opened :-

08	7			36.6
09	8			33.1
10	9			32.7
11	10	0	0	32.2
12	11			31.7
13	12			31.2
14	13			$30.8 = \Theta_3$

Determination of Mechanical equivalent of Heat.Calculations:-

$$\frac{1}{2}n = \frac{1}{2}(\theta_2 - \theta_3) = \frac{1}{2}(34 - 30.8) = \frac{1}{2} \times 3.2 \\ = 1.6^\circ\text{C}$$

$$\text{Actual temperature, } \theta = (\theta_2 - \theta_1) + \frac{1}{2}(\theta_2 - \theta_3) \\ = (34 - 29) + 1.6 = 5 + 1.6 = 6.6^\circ\text{C}$$

$$J = \frac{Vit}{(m_s + m_1 s_1)(\theta_2 - \theta_1)} = \frac{Vit}{(m_s + m_1 s_1)\theta} \\ = \frac{3.2 \times 1.6 \times 6 \times 60}{(89.5 \times 0.21 + 113.1 \times 0.41) \times 6.6} = 4.29 \text{ Joule/cal}$$

$$\text{Percentage of error} = \frac{\text{Obtained result} - \text{Actual result}}{\text{Actual result}} \times 100\% \\ = \frac{4.29 - 4.2}{4.2} \times 100\%$$

$$= 2.14\% \text{ (Approx.)}$$

Result with Explanation:

$$J = 4.29 \text{ Joule/cal}$$

We know, mechanical equivalent of heat is 4.2 Joule/cal.
 Experimental result is very near to actual result
 and percentage of error is 2.14%.

So, we can say that our experiment is correct.

Precautions:

- 1) The coil of wire should remain completely immersed in the liquid.

Determination of Mechanical equivalent of Heat.

- 2) The voltmeter should be connected across the coil with its positive pole connected to the terminal where the current enters the coil.
- 3) The positive terminal of the battery should be connected to the positive pole of the ammeter.
- 4) The ammeter and voltmeter should be examined for any zero-error.
- 5) The liquid should be stirred slowly but thoroughly.
- 6) Correction should be made for loss of heat due to radiation from the calorimeter.
- 7) Rise temperature should not be lagged.
- 8) All the connection should be tight.
- 9) The end of wire must be cleaned by sand paper.

Discussions:

- 1) The balance was old, so the weight was not correct.
- 2) There was no 10 gm, so the correct weight did not come.
- 3) The experimental liquid was mixed with other liquid, so the result did not come correct.
- 4) The thermometer was disturbed. So, the result did not come correct.
- 5) Stop-watch also disturbs to record time.

Comparison of E.M.F. of two cells using potentiometer.

PAGE NO. 06

EXPT. NO. 02

Theory:

If E_1 = E.M.F. of the first cell (E_1), E_2 = E.M.F. of the second cell (E_2), l_1 = distance of the balanced point measured from end A of the potentiometer with the cell E_1 , l_2 = distance of the balanced point measured from end A of the potentiometer with the cell E_2 , P = resistance per unit length of the wire and I = strength of current passes through the wire, then fall of potential per unit length for the cell, $E_1 = l_1 PI$.

$\therefore E_1 = l_1 PI$ and similarly, $E_2 = l_2 PI$.

$$\text{Therefore, } \frac{E_1}{E_2} = \frac{l_1 PI}{l_2 PI} = \frac{l_1}{l_2} \dots\dots\dots (1)$$

Apparatus:-


Potentiometer, one storage or standard cell (E), two experimental cells (E_1 and E_2), galvanometer (G), key (K), Commutator (K_1), variable resistor (R_h), jockey connecting wire, sand paper, blade etc.

Description of connections:

A storage cell (E) and variable resistor (R_h) is joined between A and B with a key (k). The positive terminals of the experimental cells (E_1 & E_2) are joined with A and negative terminals with two points of a commutator (K_1). One point of the galvanometer is joined to the third points of the commutator and other point of galvanometer with a jockey.

FIGURE NO. 02

Figure - 02 (Exp-02) : Comparison of E.M.F. of two cells using potentiometer.

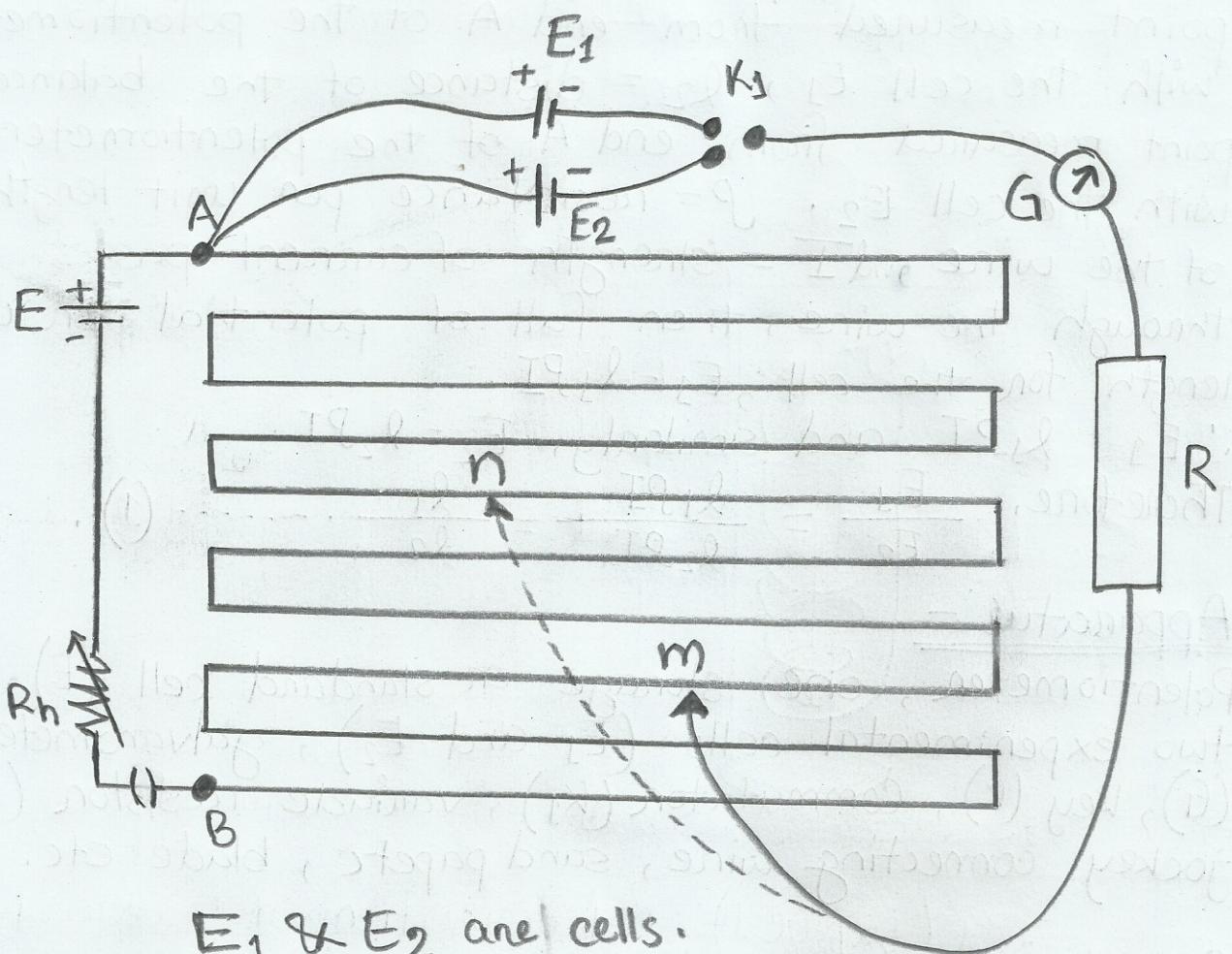

E_1 & E_2 are cells.

E = standard storage cell

K_1 = Commutator

G = Galvanometer

K = Key

R_h = Variable resistor (sometimes it is fixed inside the galvanometer)

m, n = balanced point by jockey

R = high resistance.

Figure - 02 (Exp-02) : Comparison of E.M.F. of two cells using potentiometer.

Comparison of E.M.F. of two cells using potentiometer.

Procedure:-

- 1) All the connections were made as in the figure. At first, E_1 was connected in the circuit & E_2 was kept outside of the circuit. The current was passed by connecting K and K_1 and pressing jockey the balanced point was found somewhere at m (this time galvanometer showed no deflection). The distance A to m was measured from the scale with the potentiometer. Let the distance = l_1 .
- 2) The cell E_1 was removed and E_2 was connected and similarly the balanced point n was found out and the distance A to n was measured. Let the distance = l_2 .
- 3) The resistance in the variable resistor (R_h) was changed at least three times and in each case, the length l_1 and l_2 was measured.
- 4) In each case $\frac{l_1}{l_2}$ was determined and the average was taken.

Data and Table:-

No. of observations in the variable resistor (Ω)	Resistance in the variable resistor (Ω)	Position of balanced point				$E_1 = \frac{l_1}{l_2}$	Mean $\frac{l_1}{l_2}$		
		Cell E_1		Cell E_2					
		l_1 cm	Mean l_1 cm	l_2 cm	Mean l_2 cm				
1	2	980.4		800.1		1.23			
		980.4	980.36	800.2	800.2				
		980.3		800.3					

Comparison of E.M.F. of two cells using
potentiometer.

		965.2		713.4			
2	4	965.3	965.23	713.5	713.43	1.35	1.313
		965.2		713.4			
		842.2		617.8			
3	6	841.1	841.8	617.7	617.73	1.36	
		842.1		617.7			

Calculations:

$$1) \frac{E_1}{E_2} = \frac{l_1}{l_2} = \frac{980.36}{800.2} = 1.23 : 1$$

$$2) \frac{E_1}{E_2} = \frac{l_1}{l_2} = \frac{965.23}{713.43} = 1.35 : 1$$

$$3) \frac{E_1}{E_2} = \frac{l_1}{l_2} = \frac{841.8}{617.73} = 1.36 : 1$$

Result with Explanation:

The mean ratio of $E_1/E_2 = 1.313 : 1$.

Generally, E.M.F. of dry cell is 1.5 volt. But for long days the batteries are in the laboratory; so their E.M.F. will reduce. So, the ratio of two cells will not be 1 : 1, it will be less than that. So, our experimental value is approximately correct.

Precautions:

- 1) All the positive terminals of cells should be connected to A.
- 2) The readings should be taken when the needle of the galvanometer was completely at rest.

Comparison of E.M.F. of two cells
using potentiometer.

PAGE NO. 09

EXPT. NO. 02

- 3) The key (K) and commutator (K_1) should be ON only when the reading was taken.
- 4) A high resistance (R) should be inserted in the galvanometer circuit.

Discussions:-

- 1) One cell (E_1) was not properly working. So the result was not correct.
- 2) The galvanometer sometimes disturbed, so some error come in the result.

Determination of specific resistance of a wire using meter bridge.

Theory:

The arrangement shown in the figure, if known resistance R is connected to the left gap DE and an unknown resistance X is connected to the right gap HI and for the point N if the distance of null point AN = l and LN = $(100-l)$ then by the principle of wheatstone's network,

$$\text{we get, } \frac{R}{X} = \frac{l}{(100-l)} = \frac{l}{100-l}$$

$$\text{or, } X = \frac{R(100-l)}{l} \quad \text{--- (1)}$$

where, ρ = resistance per unit length of the material of the wire of the bridge.

Now, knowing l and R , X can be calculated.

Again, from laws of resistance, we get, $X = \frac{\rho L}{A}$

$$\text{or, } \rho = \frac{XA}{L} \quad \text{--- (2)}$$

where, L = length of the wire, A be the cross section of the wire X and $A = \pi r^2$, r = radius of the wire.

Therefore, knowing X , L and A , we can calculate the specific resistance ρ .

Apparatus:

A meter bridge, cell or battery, commutator, a resistor, unknown resistance, key, connecting wires, screw gauge, meter scale, sand paper, blade etc.

FIGURE NO. 03

δh = shunt

G = Galvanometer

DE = Known Resistance R

HI = Unknown Resistance X

Battery = B K = Key

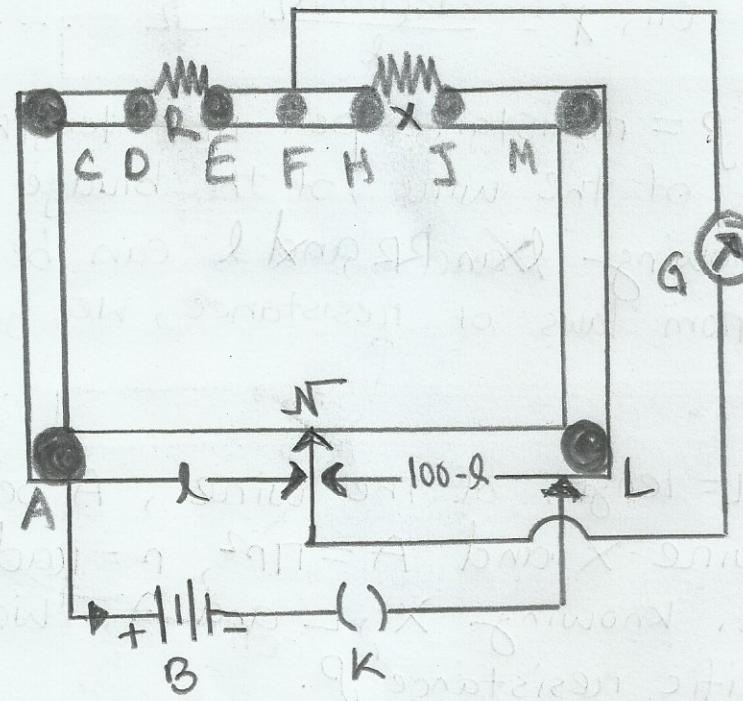


Figure - 03 (Exp - 03) : Determination of specific resistance (P) of a wire by meter bridge.

Determination of specific resistance of a wire using meter bridge.

Description of the connections:-

A battery on cell B and a key K is joined in series and is connected to the point D and I. A known resistor R is connected between D & E and an unknown resistor X is connected between H & I. One end of the galvanometer G is connected to the binding screw F and the other end with jockey. A shunt (sh) is connected with the galvanometer in parallel to save the galvanometer from destroying. Thus, we get four resistances namely AN, NL, R and X as in Wheatstone's network. Now if the circuit is completed by tapping the key K, the current will come to the point N and it will divide in to DE & DN and again will meet at the point I and will go to the battery.

Procedure:

- 1) All the terminals and the ends of the connecting wires were cleaned by sand paper.
- 2) All the connections were made as shown in the figure. A suitable resistance is placed in the resistor R and pressing the jockey on the bridge wire a null point was obtained near about the middle of the wire. By removing the shunt the null point was determined more accurately. The current was now reversed and proceeding as before the null point was again obtained and the mean was taken.

Determination of specific resistance of a wire using meter bridge.

- 3) Several sets of readings were taken similarly and x was determined and the mean value was taken.
- 4) The length (L) of the unknown resistance (x) was determined by a meter scale and the radius (r) by a screw gauge & $A = \pi r^2$ was calculated and hence P was calculated from equation no. (2).

Data and Table:-

Determination of radius by screw gauge :-

Pitch, $p = 1\text{ mm}$; Total number of circular scale division, $n = 100$.

$$\therefore \text{Least count (L.C.)} = \frac{P}{n} = \frac{1\text{ m}}{100} = 0.01\text{ mm} = 0.001\text{ cm}$$

Instrumental error = 0.

Table - 01: Determination of radius :

No. of observa- tions	Linear scale reading a	Circular scale reading x	Least count c	Value of $b = x.c$	Total observed circular reading $d' = a + b$	Average observed circular reading d'	Instru- mental error $\pm e$	Con- verted diameter $d = d' + \frac{e}{2}$ -($\pm e$)	Con- verted radius r
	cm	cm	cm	cm	cm	cm	cm	cm	cm
1	0	33	0.001	0.033	0.033				
2	0	32	0.001	0.032	0.032	0.032	0	0.032	0.016
3	0	31	0.001	0.031	0.031				

Determination of specific resistance of a wire using meter bridge.

Table - 02 : Determination of resistance:Length of the wire, $L = 56 \text{ cm}$

No. of observa- tions	Null point, l Direct current cm	Null point, l Reversed current cm	Av. null point, l cm	Resista- nce, R Ω	Resistance X Ω	Average resistance \bar{x} Ω
01	47.6	47.6	47.6	09	9.91	
02	52.8	52.8	52.8	11	9.96	9.89
03	57.0	57.2	57.1	13	9.80	

Calculations :-

1) Resistance, $X = \frac{R(100-l)}{l} = \frac{9 \times (100-47.6)}{47.6} = 9.91 \Omega$

Similarly, resistance of no. 2 and 3 are calculated.

\therefore Specific resistance, $\rho = \frac{X \pi r^2}{L} = \frac{9.91 \times 3.1416 \times (0.016)^2}{56}$

$$= \frac{7.97 \times 10^{-3}}{56}$$

$$= 1.423 \times 10^{-4} \Omega \cdot \text{cm}$$

$$= 1.423 \times 10^{-6} \Omega \cdot \text{m}$$

Result with Explanation:

Specific resistance of an unknown wire $= 1.423 \times 10^{-6} \Omega \cdot \text{m}$.

Wire is of unknown of resistance and specific resistance. So, it is not possible to find percentage of error.

Determination of specific resistance of a wire using meter bridge.

Precaution :-

- 1) The null point should be nearer to the middle of the bridge.
- 2) Current should be passed through the circuit only when readings are taken.
- 3) The connection should be tight and the terminals of the instrument and the ends of the wires must be cleaned by sand paper.
- 4) The radius should be determined very carefully.
- 5) Plugs of resistance box should be tightened.

Discussions:-


- 1) The galvanometer was very old, so the correct result was not obtained.
- 2) Due to old screw gauge, the diameter was not correctly measured.

Conversion of AC to DC using full wave rectifier using two diodes.


Theory:

When one or more diodes convert A.C. voltage into pulsating D.C. voltage, the circuit is called rectifier and the process is known as rectification. The property of semiconductor diode allows current to flow through the diode when it is forward biased and prevents the flow of current when the diode is reverse biased. This property of the diode is the base to convert alternating waveform (sinusoidal) into a unidirectional (D.C) waveform. Suppose diode resistance is R and load resistance is R_L . In case of forward biasing current flows through the diode. But during reverse bias current flowing through it is very small (mA). Rectifier is used for converting AC flow into DC flow. During the positive half cycle current flows and during negative half cycle reverse bias is established and no current flows through the diodes. To smooth DC wave, capacitor C is used in the circuit. During positive half cycle the capacitor receives charges and in negative half cycle it discharges. As a result, between two DC halves the wave becomes smooth. This action of smoothing is called filtering. By a DC voltmeter, DC voltage between the resistor R_L is measured and current is measured by DC ammeter. In oscilloscope screen between the two terminals of the resistance, DC flow is observed. Circuit, connecting terminal, and input and output signals etc are shown in figures a and b.

FIGURE NO. 04

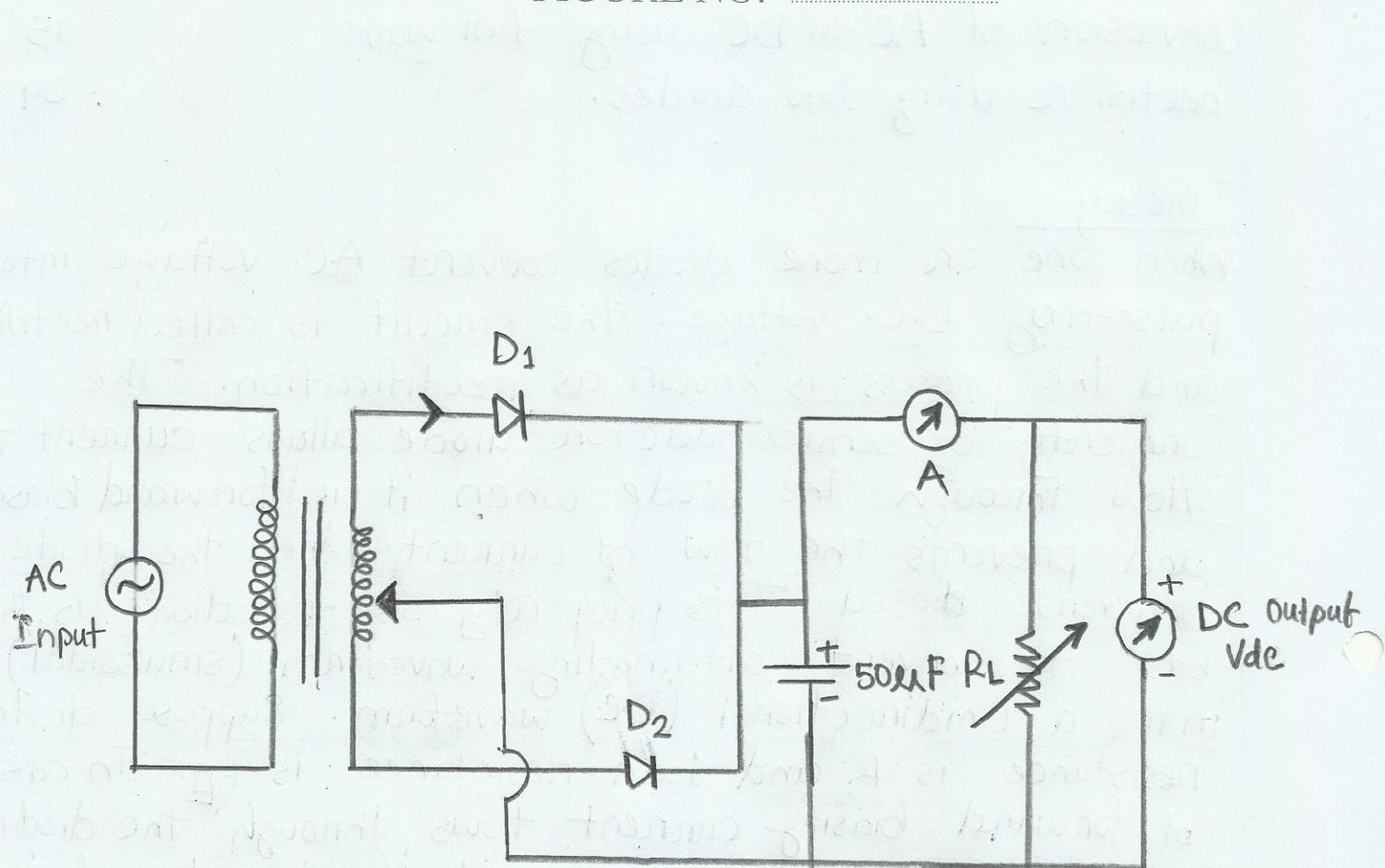

(a)

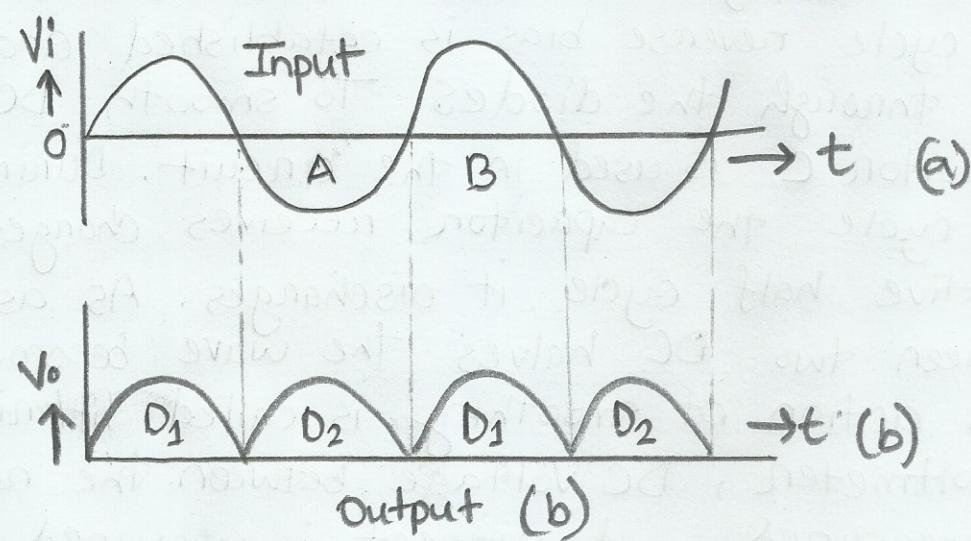

Output (b)

Figure - A (Exp-04): Full wave rectifier.

Conversion of AC to DC using full wave rectifier using two diodes.

Instruments and Materials Required:-

Secondary / step down transformer, two diodes (D_1 , D_2), load resistor ($R_L = 10 - 100 \Omega$), connecting wires, soldering wires and heater/iron, soldering board, oscilloscope, DC voltmeter, AC millimeter, capacitor ($C = 50 \mu F$), project boards etc.

Full Wave Rectifier:

Procedure:

- 1) Two diodes were connected with the upper and lower output terminals of the transformens as per the diagram.
- 2) Negative terminals of the two diodes were connected combinedly.
- 3) A capacitor (C), a load resistor (R_L), a DC voltmeter were connected in parallel and an ammeter was connected in series and central point the transformer was connected to R_L , C and lower terminal of the voltmeter. The lower terminal of C and R_L were connected to the ground.
- 4) The mid-point of the negative terminal of the diode was connected to the capacitor by a wire.
- 5) By flowing current in the circuit, current and output are measured.
- 6) Output DC voltage and current were observed by oscilloscope.
- 7) A graph of V_{dc} versus I_{dc} was plotted and it was a straight line that passes through the origin.

Conversion of AC to DC using full wave rectifier using two diodes.

Experimental data & Table:-

1) Capacitance of the capacitor, $C = 50 \mu F$.

2) Resistance of the diode, $R = 1.5 \Omega$

3) $I_{dc} = \frac{2I_m}{\pi}$, I_m = peak value of current.

Table:-

No. of Observations	Load Resistance $R_L \Omega$	Input Voltage V_{in} Volt (AC)	Peak value of current I_m Amp (AC)	$I_{dc} = \frac{2I_m}{\pi}$	V_{dc} Volt
01	2	7.4	8.0	5.1	7.4
02	4	9.4	10.36	6.6	9.4
03	6	10.5	11.15	7.1	10.5
04	8	12.1	12.87	8.2	12.1

Observation:

Output voltage has been observed by the oscilloscope and V_{dc} is measured by voltmeter.

Result:

AC wave is converted to DC wave in rectifier.

Precautions:

- 1) Circuit elements should be connected carefully.
- 2) Positive terminals of capacitor, milliammeter and voltmeter should be jointly connected.
- 3) Resistance of the resistor should be chosen carefully to fulfil the experiment.

FIGURE NO. 04

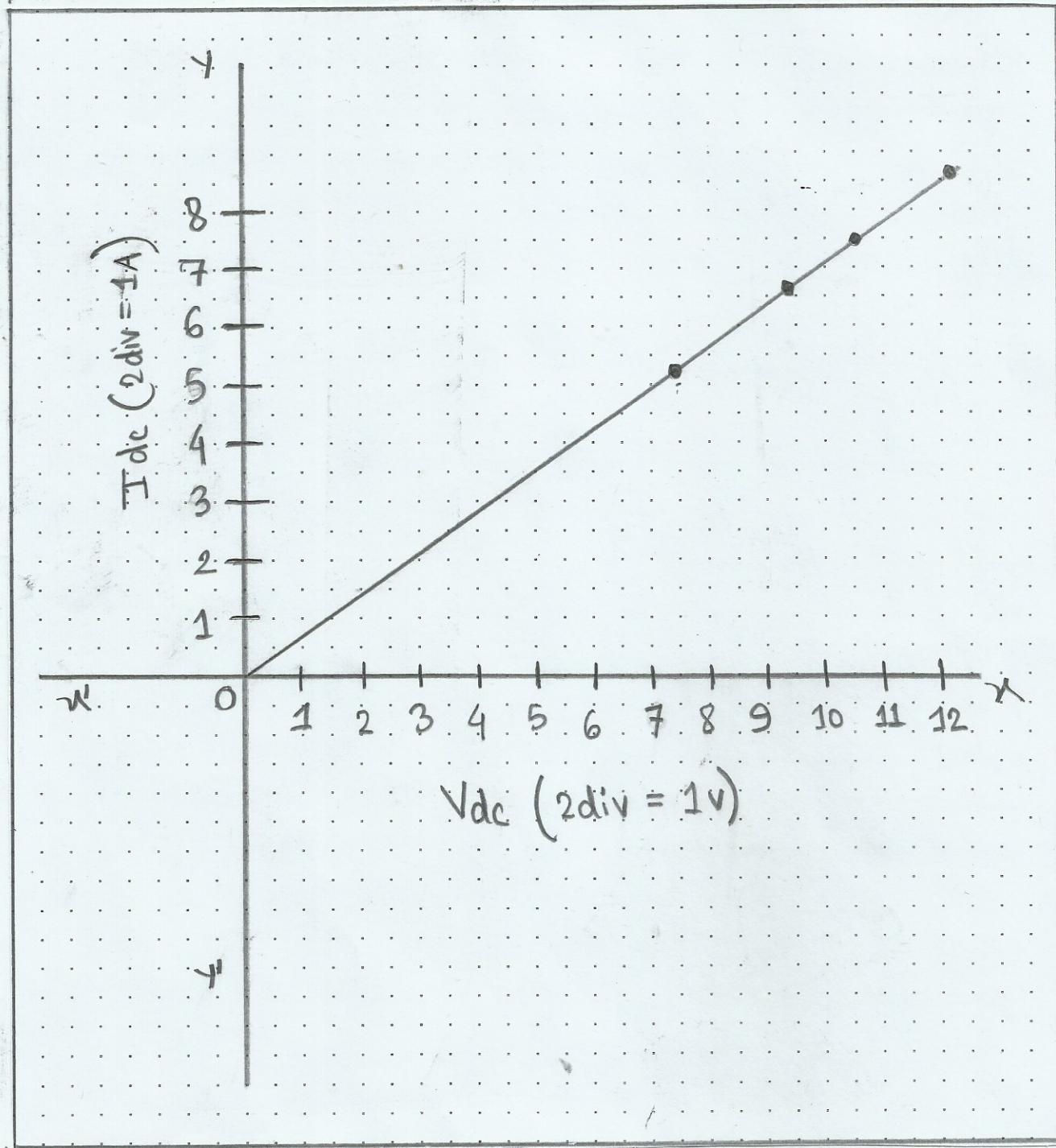


Figure - A (Exp-04): V_{dc} vs I_{dc} graph.

Conversion of AC to DC using full wave rectifier using two diodes.

- 4) Secondary / step down transformer should be taken carefully.
- 5) At the time of biasing , care should be taken also.
- 6) Input voltage should be kept 8-12 volt.
- 7) Capacitor should be used to get smooth DC output.
- 8) Secondary/ step down transformer must be used otherwise you may be shocked.
- 9) D_1 and D_2 should be taken of same value .

Discussions:

Output resistor (R_L) was connected in parallel between the two terminals A, B. If AC voltage is more than 8V to 12V, the oscilloscope may be damaged. Toys can be run with this rectifier.

Conversion of AC to DC using full wave by bridge rectifier (4 Diodes).

Theory:

When one or more diode converts AC voltage into pulsating DC voltage, the circuit is called rectifier and the process is known as rectification. There are two types of rectifiers; viz - half wave and full wave rectifier.

In full wave, rectification for both half of the input AC voltage current flows through load resistance in one direction. For one half of the input voltage, a pair of diodes become forwardly biased, when the other pair of diodes remain in reverse biased. Again for the second half of AC input voltage, the first two diodes become reverse biased and the second two diodes become forward biased. So, the current flows through the load in one direction.

In this way, in both halves of the AC input voltage across the load is produced in one direction. This DC output is not smooth DC but pulsating DC i.e. both AC and DC components are present in the output. In order to get pure DC voltage, the output is smoothed by a filter circuit.

Instruments and Materials Required:

Step down transformer, bridge rectifier (4 diodes), capacitor (300 or 50 μ F), resistor ($R_L = 10-100 \Omega$), multi-meter or oscilloscope, connecting wires, AC power supply, project board etc.

FIGURE NO. 04

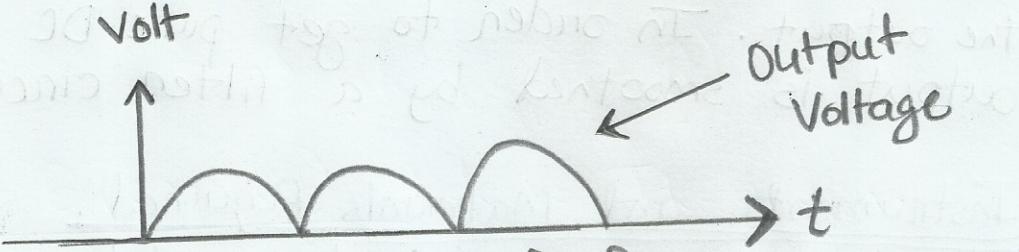
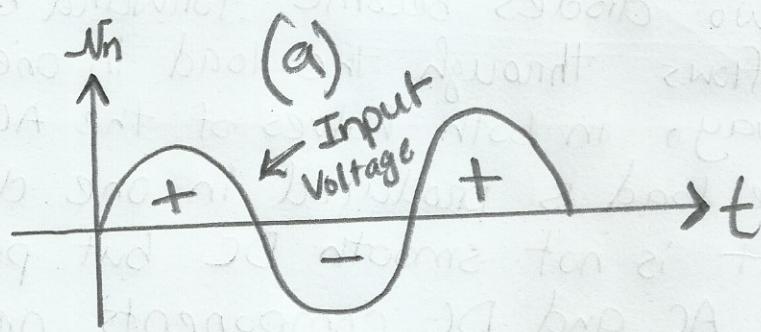
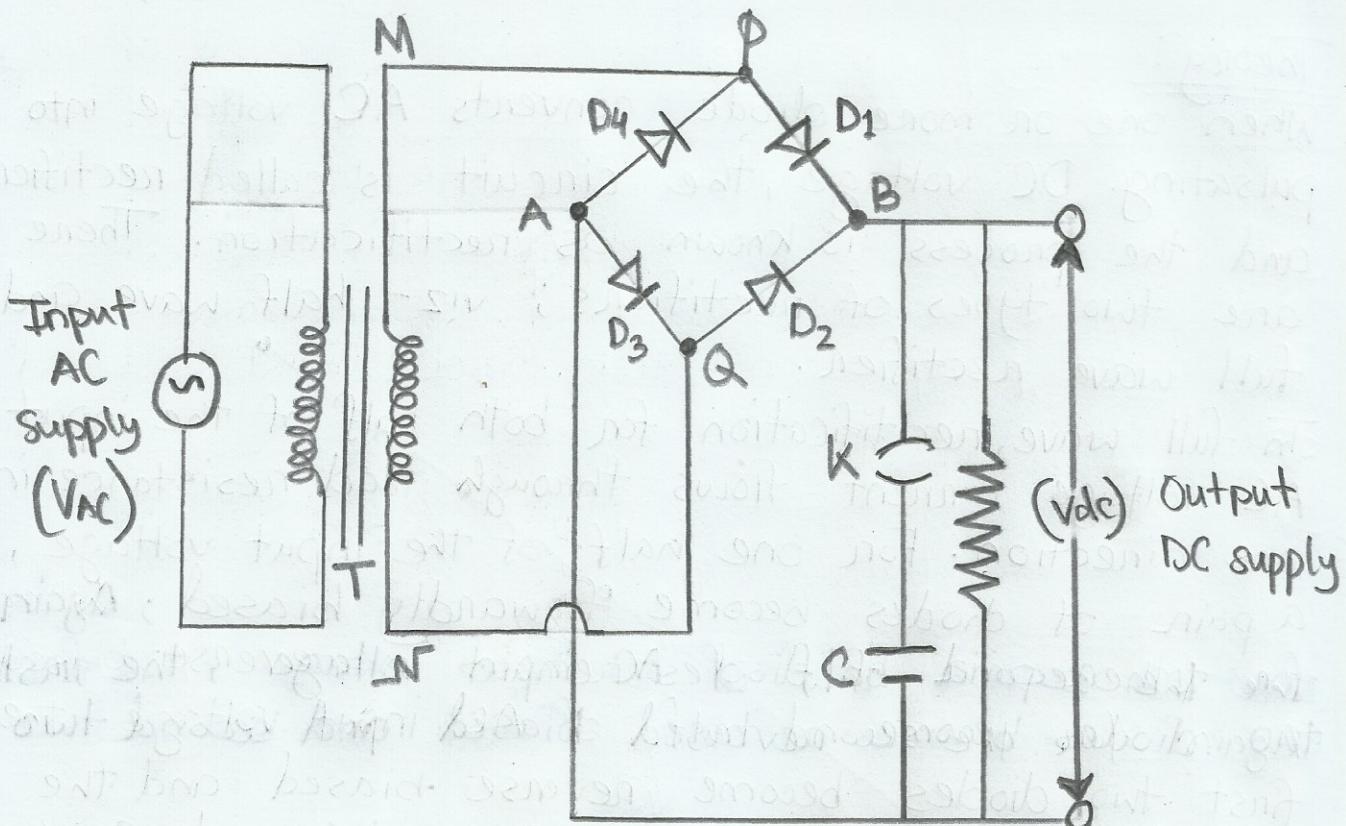


Figure-B (Exp-04): Full wave bridge rectifier.

Conversion of AC to DC using full wave by bridge rectifier (4 Diodes).

Connection of circuit:-


To construct a full wave bridge rectifier, we need four diode. Four diodes D_1 , D_2 , D_3 and D_4 are connected to form a bridge as shown in figure.

The AC supply to be rectified is applied diagonally to opposite ends of the bridge through the transformer. Between other two ends of the bridge, the load resistance R_L is connected.

Procedure:

- 1) During positive half cycle of the secondary voltage M terminal of the transformer becomes positively charged and N terminal becomes negatively charged. In this situation, diodes D_1 and D_3 becomes forward biased and diodes D_2 and D_4 become reverse biased. So, along MPD_1BAD_3QN current flows and across R_L potential drops. Again during negative half cycle terminal M becomes negatively charged. So, along NQD_2BAD_4PM path current flows will be seen that current through load R_L flows always in the same direction.
- 2) Wave shapes of the input and output are observed through the oscilloscope. Input and output will be observed as in figures (a) and (b).
- 3) Voltage across R_L measured by the help of oscilloscope. If oscilloscope is not available, AC/DC voltage can be measured by a voltmeter.
- 4) A graph of V_{dc} versus I_{dc} was plotted and it was a straight line passes through the origin.

FIGURE NO. 04

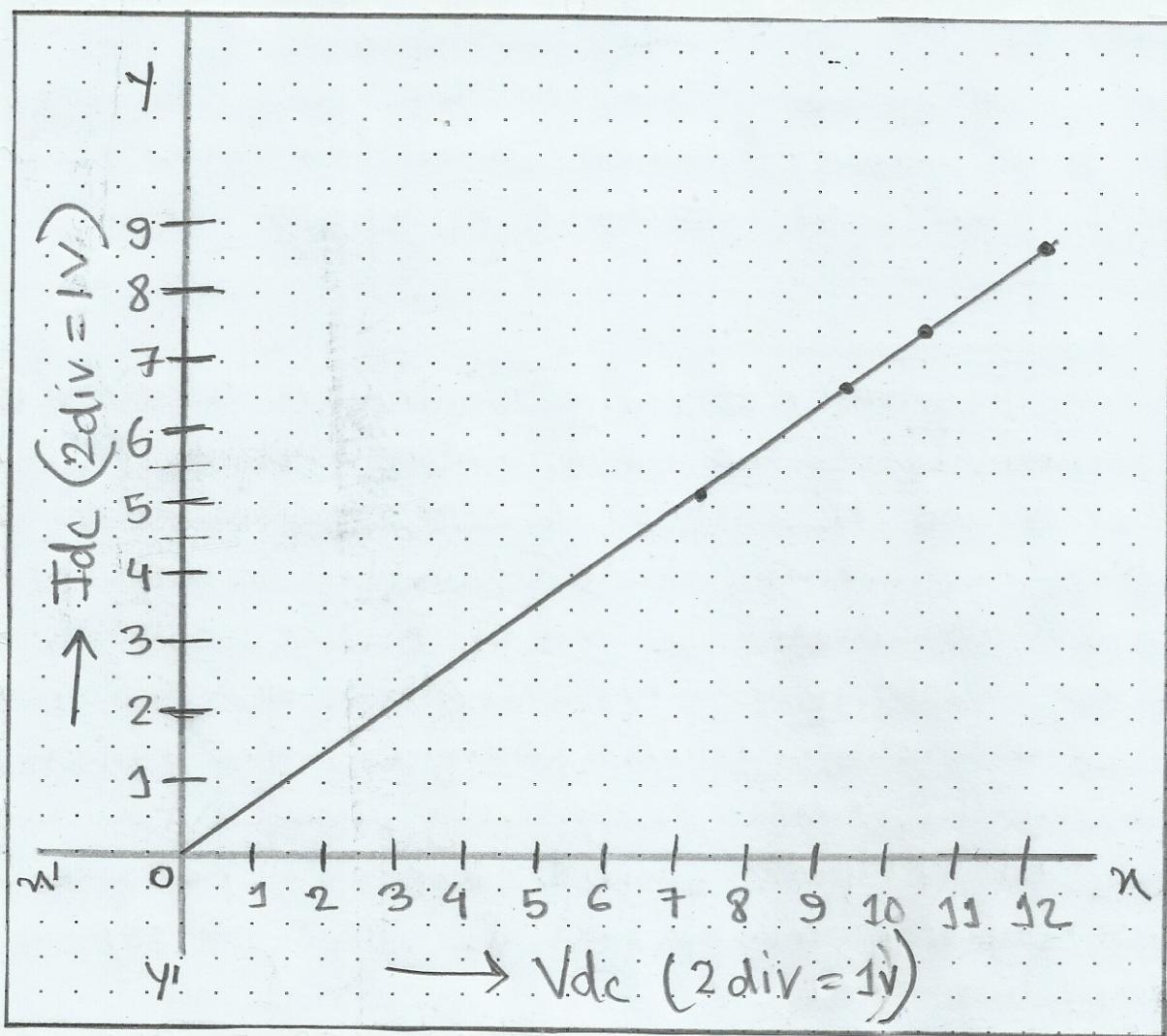Figure-B (Exp-04): V_{dc} vs I_{dc} graph.

Conversion of AC to DC using full wave
by bridge rectifier (4 diodes).

Experimental Data and Table:-

- 1) Capacitance of the capacitor, $C = 50 \mu F$
- 2) Resistance of the diode, $R = 1.5 \Omega$
- 3) Load resistance, $R_L = 2, 4, 6, 8 \Omega$
- 4) $I_{dc} = \frac{2I_m}{\pi}$, I_m = peak value of current.

Table:-

No. of Observa- tions	Load Resistance R_L Ω	Input Voltage V_{in} Volt (AC)	Peak value of current I_m Amp (AC)	$I_{dc} = \frac{2I_m}{\pi}$	V_{dc} Volt
01	2	7.4	8	5.1	7.4
02	4	9.4	10.36	6.6	9.4
03	6	10.5	11.15	7.1	10.5
04	8	12.1	12.87	8.2	12.1

Observation:-

Output voltage been observed by the oscilloscope
and V_{dc} is measured by Voltmeter.

Result:-

AC wave is converted to DC wave; so wave is
rectified.

Precautions:-

- 1) Connection of the diode should be correct.
- 2) Terminals of the wires should be made tight.

Conversion of AC to DC using full wave by bridge rectifier (4 diodes).

4) Step down transformer should be used.

Discussions:

1) Between the other two end of the bridge, the resistance R_L is connected. If R_L voltage is more than 12 V, the oscilloscope may be damaged. Taps and where dry cells are used, This bridge rectifiers are connect.

Theory:-

A digital circuit having one or more input signal but only one output signal is called gate. These circuits are designed to process digital signals and there are a number of standard unit "logic gates" are available. There are 7 logic gates viz. - AND, OR, NOT, NAND, NOR, X-OR and X-NOR gate. Among them, there are only 3 basic gates viz. AND, OR and NOT gate. In most cases, diodes and transistors are used to construct logic gates. Using integrated circuit (i.e. semiconductors), we will describe working procedure of three gates (AND, OR and NOT gate).

A. Verification of AND gate activity (Truth table) using integrated circuit (IC) objectives:-

Verification of the operation of an AND gate by IC 7408.

Theory:-

The special electronic circuit by which Boolean algebra can be materialized is known as logic gate. The logic gate which has got two or more inputs but one output and if high voltage is given to both of its inputs, the output voltage will also be high otherwise the output voltage is low, this logic gate is called AND gate. If inputs of AND gate be A & B and output is C, then $C = A \cdot B$

FIGURE NO. 05

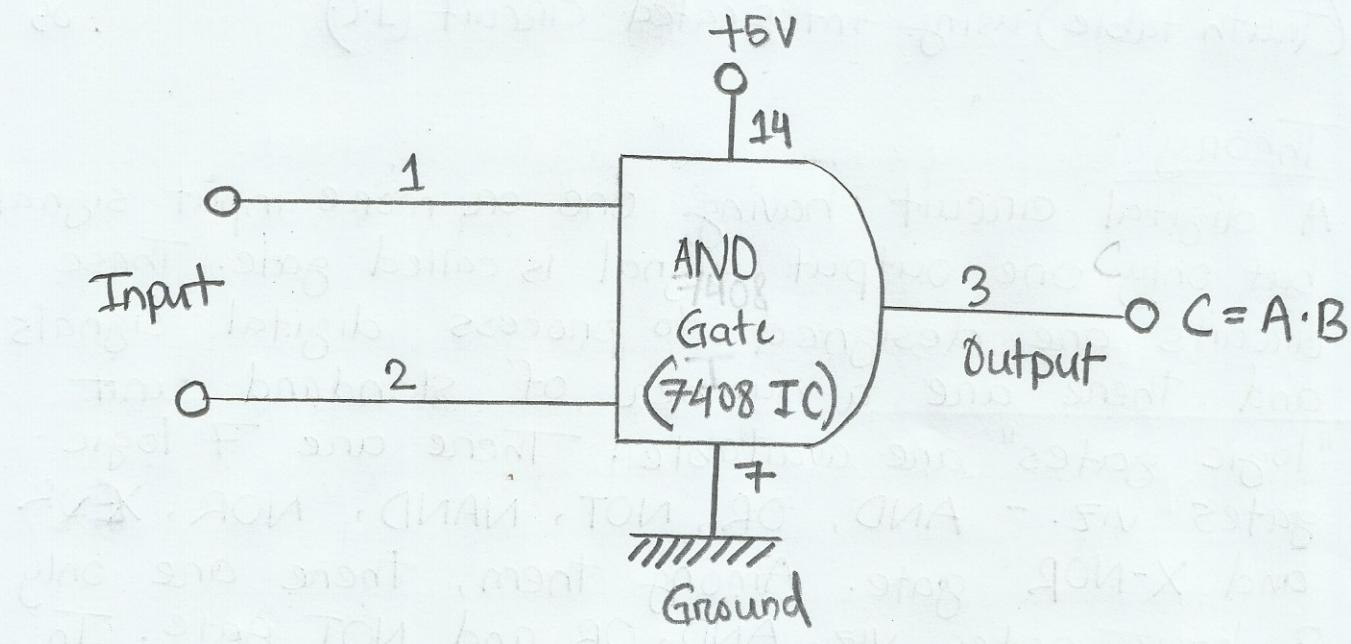


Figure - 1(A): I.C connection of AND gate
(Fundamental figure of AND gate)

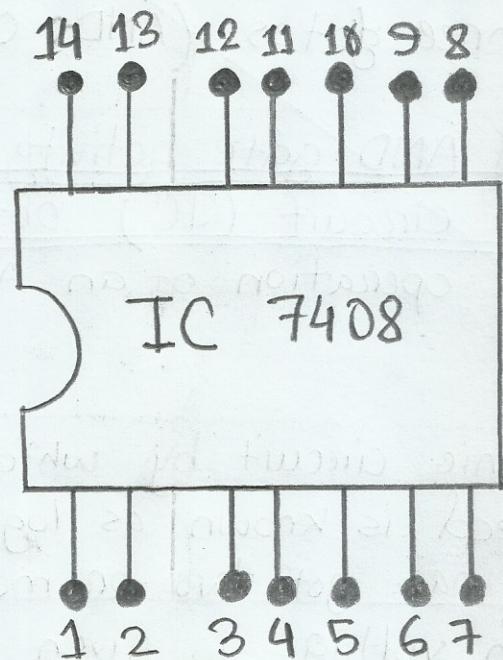


Figure - 2(A): Pin view of I.C. 7408

Apparatus and Materials:-

Digital trainer board - 1 piece , two input AND gate, 7408 I.C. - 1 piece, LED lamp or voltmeter, switch, digital multimeter, connecting wires, power supply +5V etc.

Circuit Connection:-

The IC (7408) figure and truth table of AND gate has been shown in figure-03. In an IC (7408) of AND gate, there are four AND gates each having two input and one output. The IC has 14 pins, seven on each side. Pin no. 14 is connected with +5V power supply and pin no. 7 is grounded. The inputs of first AND gate are connected with pin no. 1 and 2 and the output with pin no. 3, inputs of second AND gate are connected with pin no. 4 and 5 and output with pin no. 6. The inputs of third AND gate are connected with pin no. 9 and 10 and the output with pin no. 8. Similarly, the inputs of the fourth AND gate are connected with pin no. 12 & 13 and the output with the pin no. 11. Here, we shall use the first AND gate only.

Procedure:-

- 1) IC was placed on the trainer board according to the pin connection. Switch A and B were connected with pin 1 and 2 and pin 7 was connected

FIGURE NO. 05

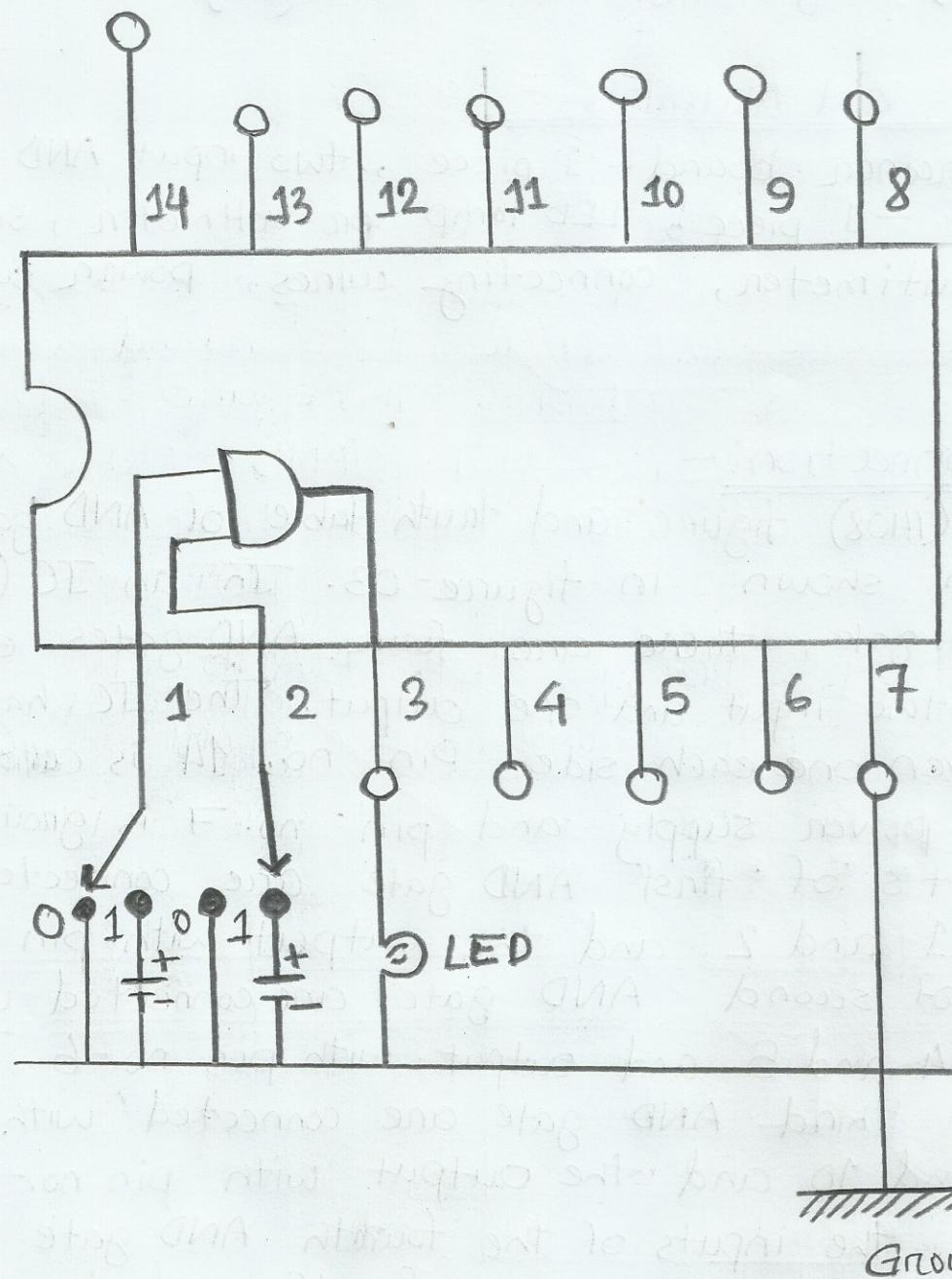


Figure - 3(A): Function of AND gate in I.C. (7408).

NAME OF THE EXPERIMENT Verification of the function of AND, OR and NOT gate circuit (Truth table) using integrated circuit (I.C.).

DATE 25/04/2022

PAGE NO. 25

EXPT. NO. 05

to the base (ground) and pin 14 was connected with +5V. Pin 3 was connected to the LED on voltmeter.

- 2) Electric connections in the trainer board were made.
- 3) Now according to the truth table, in case of IC connections, states of switches i.e. ON-OFF states were made and output i.e. state of LED was observed.

Logic conditions:-

'0' = 0V and '1' = +5V.

Observation :

AND Gate Activity		
A	B	$C = A \cdot B$
Low	Low	LED does not illuminate
Low	High	LED does not illuminate
High	Low	LED does not illuminate
High	High	LED illuminates

Truth Table		
A	B	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Result :

The AND gate truth table was verified.

Precautions:

- 1) All the connections should be made carefully and firmly in the trainer board.
- 2) Care should be taken while putting the I.C to the trainer board so that the pins of the the do not bend or break.

- 3) Care should be taken so that the voltage from the power supply should not cross +5 V.
- 4) Pin no. 14 should be connected with +5V in the trainer board.
- 5) Switches should be made OFF and ON slowly.

Discussions:-

Observing the function of AND gate i.e. seeing the ON and OFF of LED, it can be said that the I.C 7408 is connect. So, we can say that the truth table of I.C. 7408 AND gate is fulfilled.

B. Verification of OR gate activity (Truth table) using integrated circuit (I.C.) objectives:-

Verification of the operation of an OR gate by IC 7432.

Theory:

The logic gate which has got two or more inputs but one output and if any of the input voltage is high, the output will also be high, otherwise the output voltage is low, this logic gate is called OR gate. If the input of OR gate be A & B and output is C then, $C = A + B$. Here, + sign does not mean addition. The meaning of this + sign is OR operation.

FIGURE NO. 05

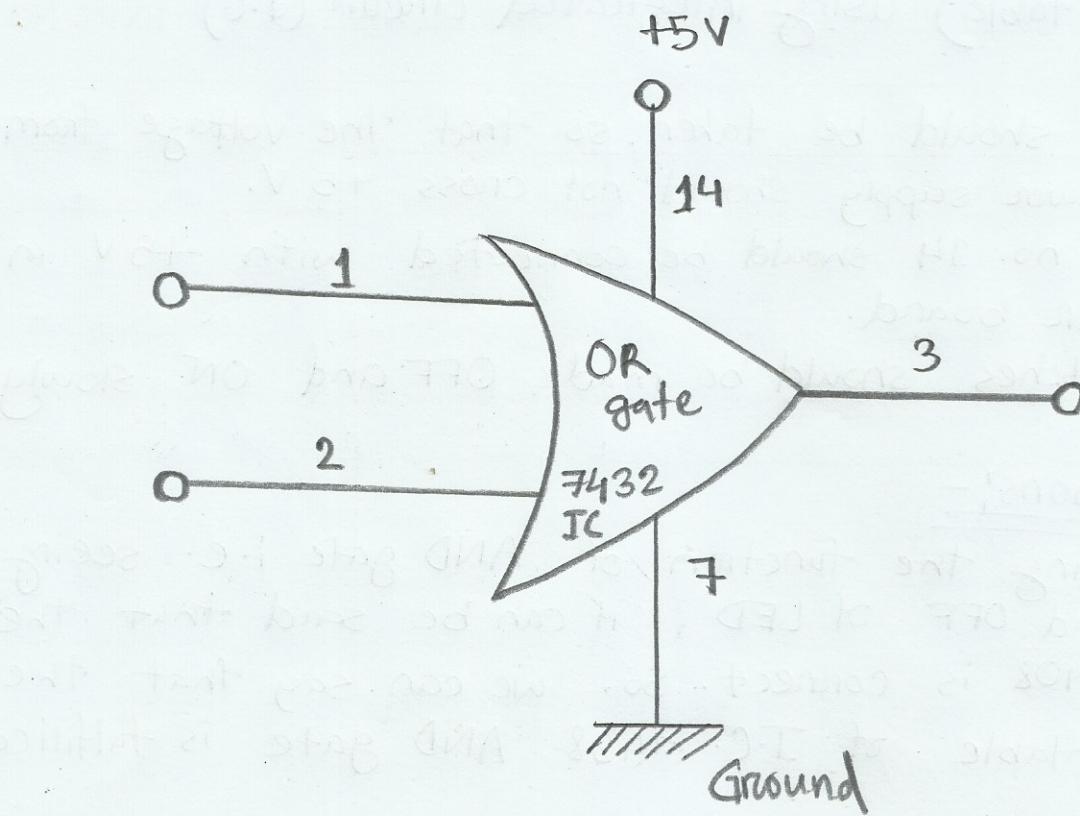


Figure - 1 (B): I.C. connection of OR gate.
(Fundamental figure of OR gate)

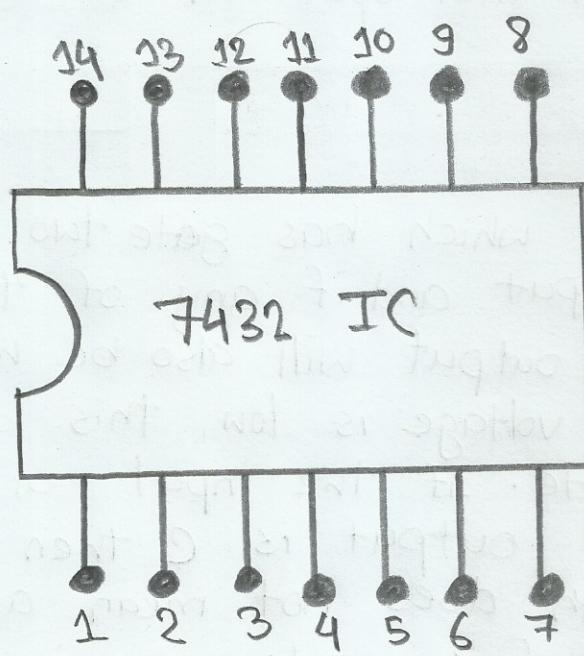


Figure - 2 (B): Pin view of I.C. 7432.

Apparatus & materials:-

Digital trainer board -1 piece, 2 input OR gate, 7432 IC - 1 piece, LED lamp or voltmeter, switch, digital multimeter, connecting wires, power supply +5V etc.

Circuit connections:-

The IC (7432) figure and truth table of OR gate have been shown in figure-3. In an IC (7432) of OR gate, there are four OR gates each having two inputs and one output. The IC has 14 pins, seven on each side. Pin no. 14 is connected with +5V power supply and pin no. 7 is grounded. The inputs of first OR gate are connected with pin no. 1 and 2 and output is connected with pin no. 3. Inputs of second OR gate are connected with pin no. 4 and 5 and output with pin no. 6. The inputs of third OR gate are connected with pin no. 9 and 10 and output with pin no. 8. In a similar way, the inputs of fourth OR gate are connected with pin no. 12 and 13 and the output with pin no. 11. Here, we shall use the first OR gate only.

Procedure:

- 1) 7432 IC is placed on the trainer board according to the figure.

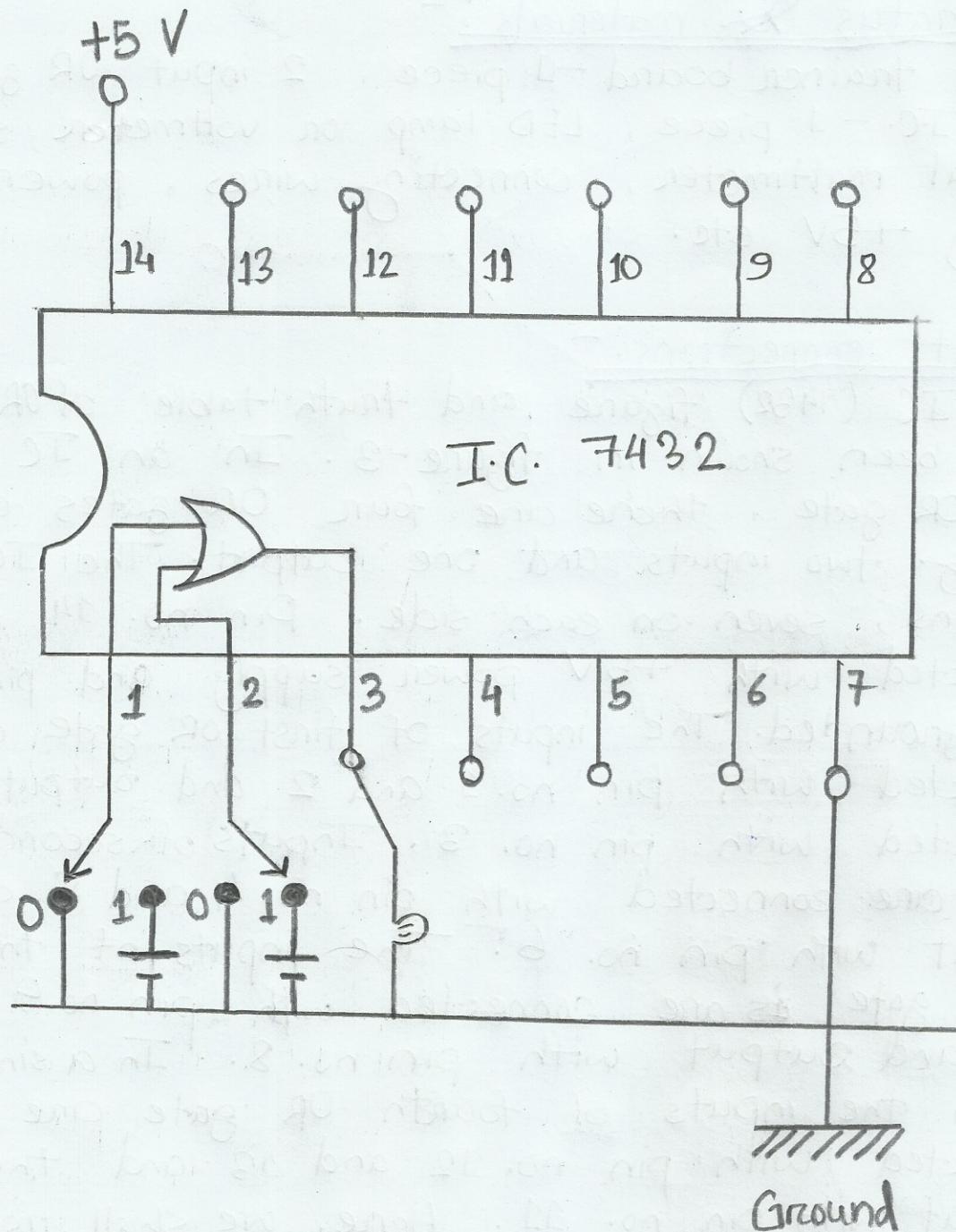


Figure - 3(B): Function of OR gate in IC 7432.

NAME OF THE EXPERIMENT Verification of the function of AND, OR and NOT gate circuit (Truth table) using integrated circuit (I.C.).

DATE 26/04/2022

PAGE NO. 28

EXPT. NO. 05

- 2) Pin no. 1 and 2 were connected with A and B, pin no. 7 was connected with the base (ground), pin no. 14 was connected with +5 V. Pin no. 3 was connected with LED which was on the trainer board or Voltmeter.
- 3) By making the switch OFF and ON, verification of output was made.
- 4) In I.C., there are four sets (A, B) inputs and four output (C). For any one set, the operation of OR gate was noted by observing the state of LED lamp.

Logical conditions:

'0' = 0 V and '1' = +5 V.

Observation:-

OR Gate Activity		
A	B	$C = A + B$
Low	Low	LED does not illuminate
Low	High	LED illuminates
High	Low	LED illuminates
High	High	LED illuminates

Truth Table		
A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Result:-

The OR gate truth table was verified.

function of AND, OR and NOT gate circuit
(Truth table) using integrated circuit (I.C.).

Precautions:-

- 1) All the connections should be made carefully and firmly in the trainer board.
- 2) Care should be taken while putting the I.C. to the trainer board so that the pins of the I.C. do not break or bend.
- 3) Care should be taken so that voltage from the power supply should not cross +5 V.
- 4) Pin no. 14 should be connected with +5 V in the trainer board.
- 5) Switches should be made OFF and ON slowly.

Discussions:-

Observing the function of OR gate i.e. seeing the ON and OFF of LED, it can be said that the I.C. 7432 is correct. So, we can say that the truth table of I.C. 7432 OR gate is fulfilled.

C. Verification of NOT gate activity (Truth table)
using integrated circuit (I.C.) objective:-

Verification of the operation of a NOT gate by I.C. 7404.

Theory:

The special electronic circuit by which boolean algebra can be materialized is known as logic gate. The logic gate which has one input and one output and if high voltage is given to the input, low voltage is obtained at the output and supply of low

FIGURE NO. 05

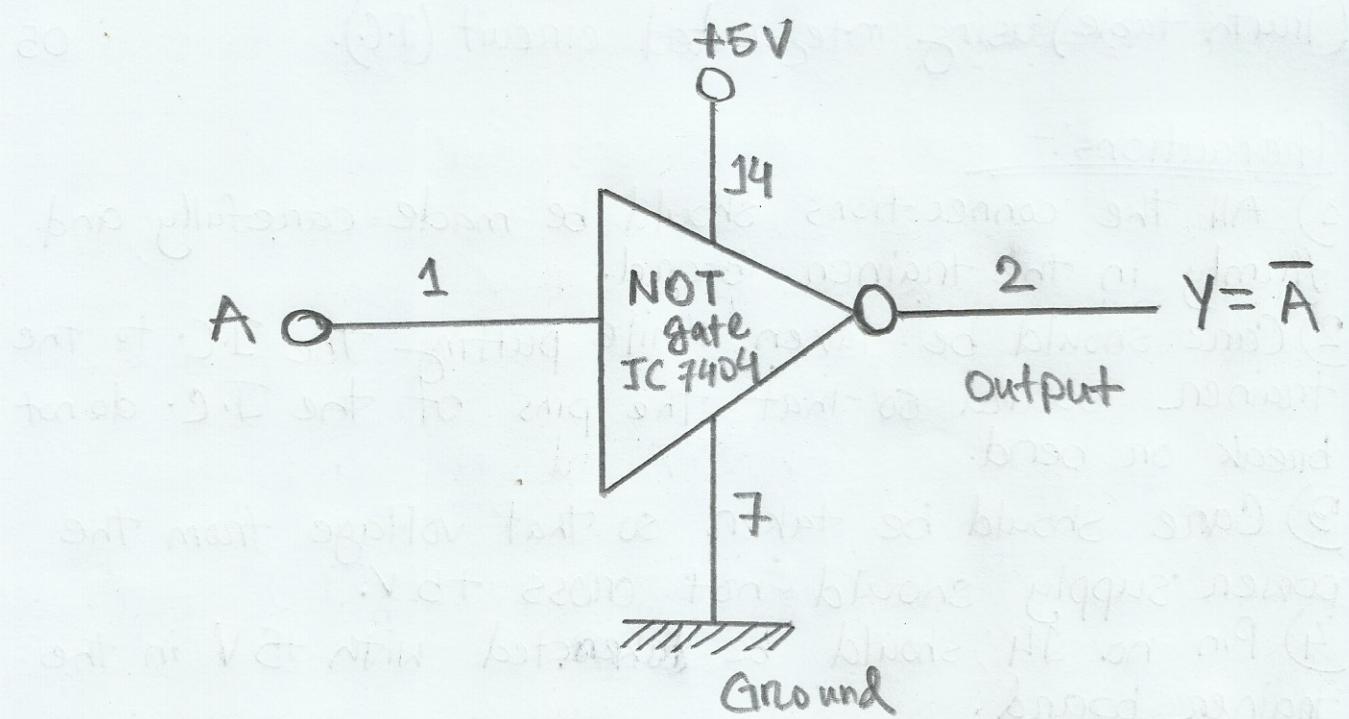


Figure - 1 (c): I.C. connection of NOT gate.
(Fundamental figure of NOT gate.)

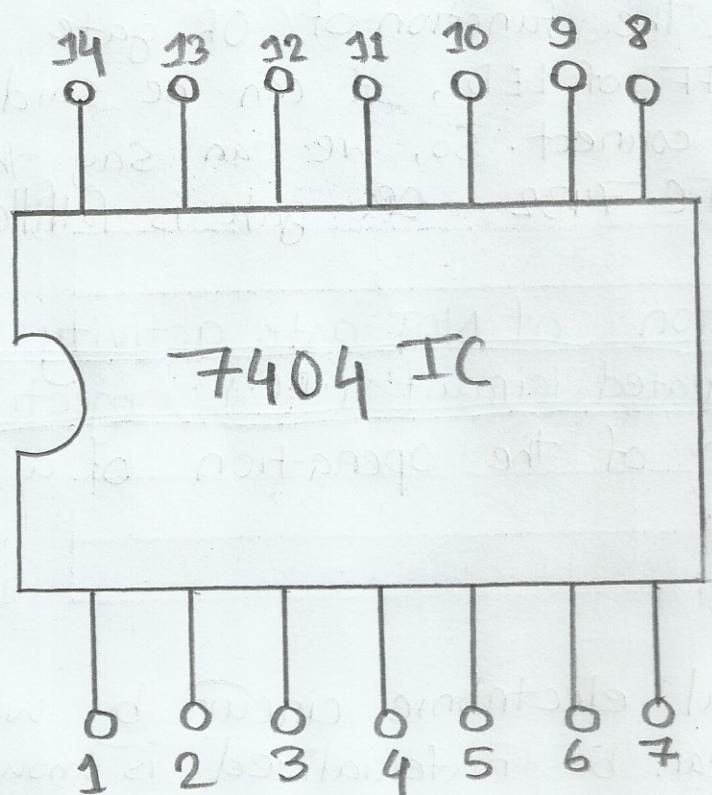


Figure - 2 (c): Pin view of I.C. 7404.

function of AND, OR and NOT gate circuit
(Truth table) using integrated circuit (I.C.).

voltage at input results in high voltage at the output, this logic gate is called NOT gate or inverter. If input of a NOT gate is A and output is y then, $y = \bar{A}$.

Hence, \bar{A} is not mathematical mean, it means the NOT operation.

Apparatus & Materials:-

Digital trainer board - 1 piece, 1 input NOT gate, IC 7404 - 1 piece, LED lamp or voltmeter, switch, Digital multimeter, connecting wires, power supply +5V etc.

Circuit connections:-

The I.C. (7404) figure and Truth table of NOT gate have been shown in figure-3. In a IC (7404) of NOT gate, there are six NOT gates each having one input and one output. IC has 14 pins, seven on each side. Pin no. 14 is connected with +5V power supply and pin no. 7 is grounded.

Inputs are connected to pin no. 1, 3, 5, 9, 11 and 13 respectively and the outputs are connected to the pin no. 2, 4, 6, 8, 10 and 12 respectively.

Hence, we shall use only input pin 1 and output pin 2. One LED is connected to the output pin no. 2.

FIGURE NO. 05

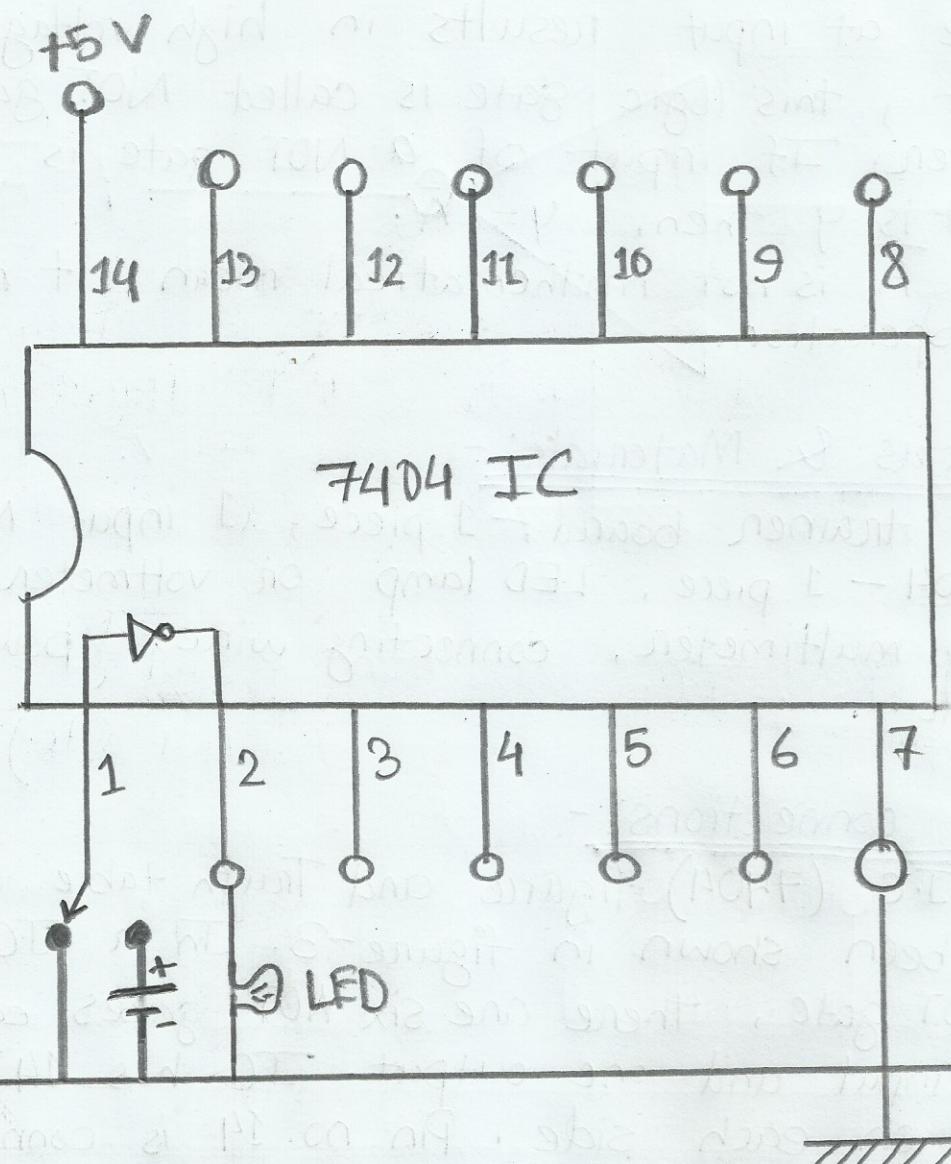


Figure - 3(c): - Function of NOT gate
in I.C. 7404.

function of AND, OR and NOT gate circuit
(Truth table) using integrated circuit (I.C.).

Procedure:

- 1) 7404 IC was placed on the trainer board according to the pin connection.
- 2) Pin no. 1 was connected with a switch, pin no. 7 was connected with base (ground) and pin no. 14 was connected with +5V. Pin no. 2 was connected with the LED on the trainers board or voltmeter.
- 3) Now, in case of IC connected, following the truth table, switch was made OFF-ON and state of the LED lamp was observed.

Logical Conditions:

'0' = 0 V and '1' = +5 V.

Observation:

NOT Gate Activity	
A	Y
Low	LED illuminates
High	LED does not illuminate

Truth Table	
A	Y
0	1
1	0

Result:

The NOT gate truth table was verified.

Precautions:

- 1) All the connections should be made carefully and firmly in the trainer board.

NAME OF THE EXPERIMENT Verification of the DATE 27/04/2022
function of AND, OR and NOT gate circuit PAGE NO. 32
(Truth table) using integrated circuit (I.C.). EXPT. NO. 05

- 2) Care should be taken while putting the I.C. to the trainer board so that the pins of the I.C. do not break on bend.
- 3) Care should be taken so that the voltage from the power supply should not cross +5V.
- 4) Pin no. 14 should be connected with +5V in the trainer board.
- 5) Switches should be made OFF and ON slowly.

Discussions:-

Observing the function of NOT gate i.e. seeing the ON and OFF of LED, it can be said that the I.C. 7404 is correct. So, we can say that the Truth table of I.C. 7404 NOT gate is fulfilled.